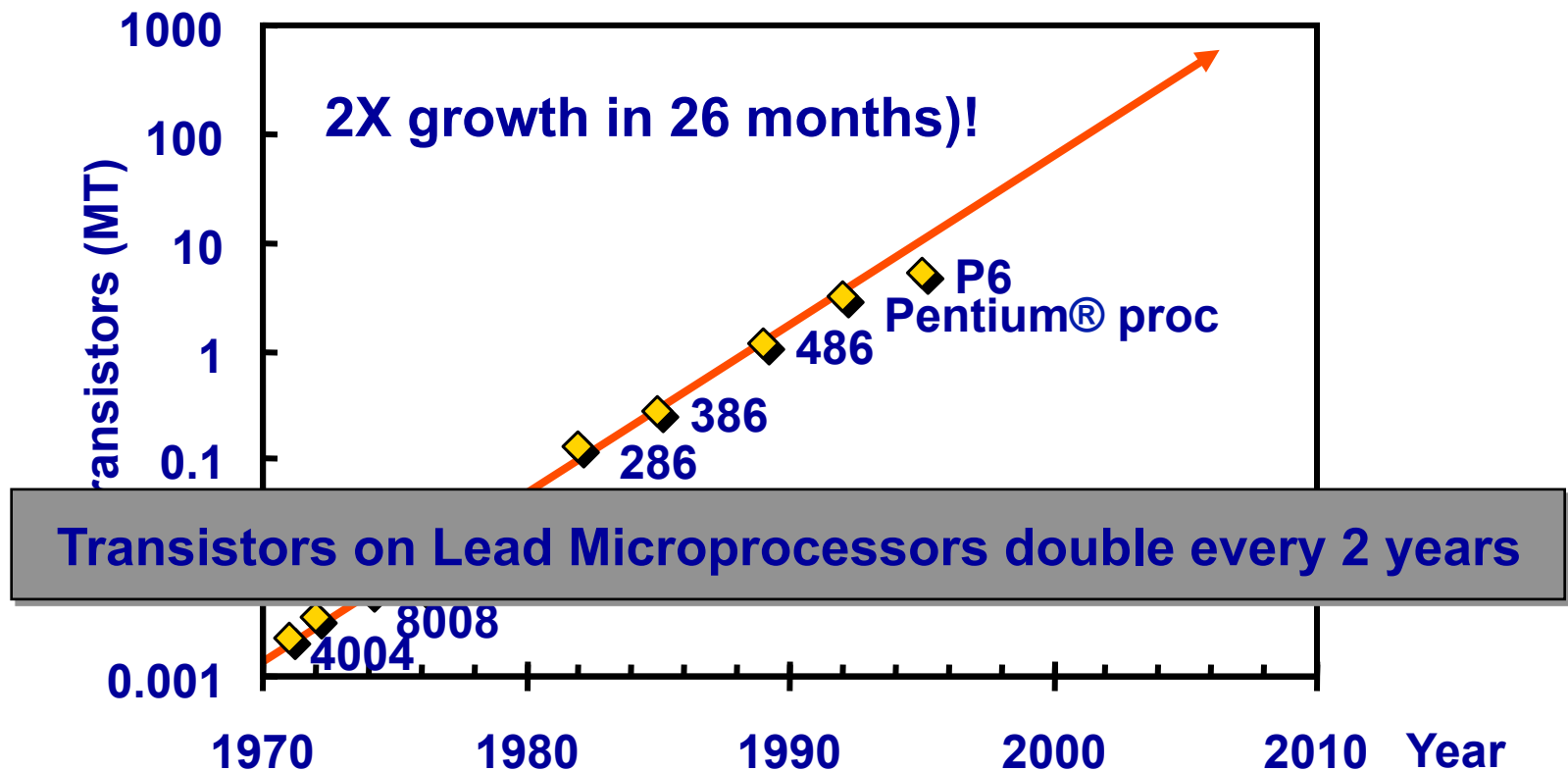


1. Introduction-Homework

- 1-1 Extrapolating the data from figure, predict the transistor count of a microprocessor in 2010



Homework

- 1-2 sketch a transistor-level schematic for a CMOS 4-input NOR gate
- 1-3 sketch a transistor-level schematic for a single-stage CMOS logic gate for each of the following functions:

$$\text{a) } Y = \overline{A + BC + D}$$

$$\text{b) } Y = \overline{A + BCD}$$

Homework

- 1-4 sketch a transistor-level schematic of a CMOS 2-input XOR gate. You may assume you have both true and complementary versions of the inputs available
- 1-5 Sketch a stick diagram for a CMOS 3-input NOR gate
- 1-6 estimate the area of 1-5

Homework

- 1-7 sketch transistor-level schematic of the following logic functions. You may assume you have both true and complementary versions of the inputs available
 - a) 2:4 decoder defined by

$$Y_0 = \overline{A_0} \cdot \overline{A_1}, Y_1 = A_0 \cdot \overline{A_1}$$

$$Y_2 = \overline{A_0} \cdot A_1, Y_3 = A_0 \cdot A_1$$

- b) 3:2 priority encoder defined by

$$Y_0 = \overline{A_0} \cdot (A_1 + \overline{A_2})$$


$$Y_1 = \overline{A_0} \cdot A_1$$

Homework

- 1-8 Use a combination of CMOS gates(represented by their symbols) to generate the following functions from A, B, and C
 - a) $Y = A$ (buffer)
 - b) $Y = A\bar{B} + \bar{A}B$ (XOR)
 - c) $Y = AB + \bar{A}\bar{B}$ (XNOR)
 - d) $Y = AB + BC + AC$ (SUM)


Homework

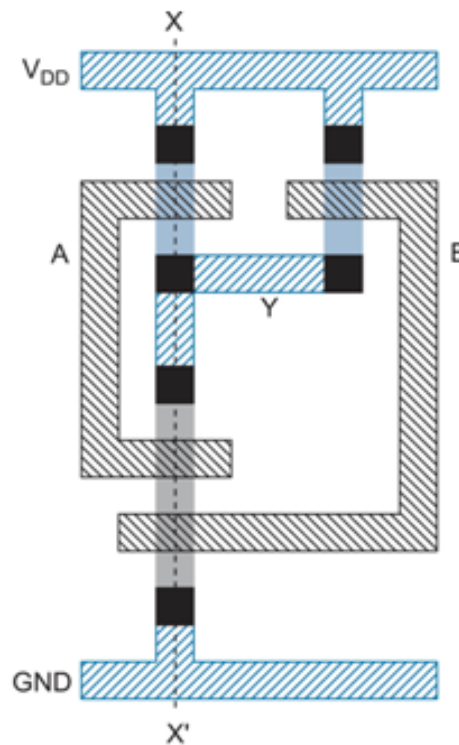- 1-9 sketch a side view(cross section) of the gate from X to X'



Home work

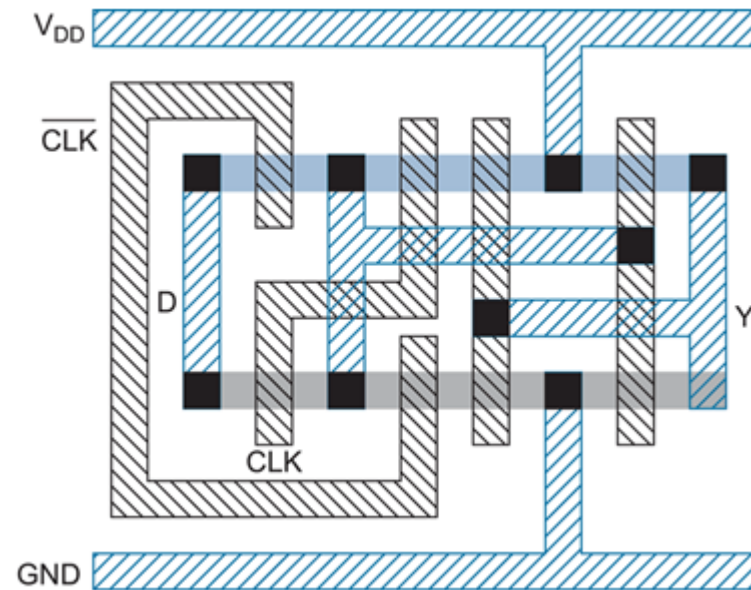- 1-10 translate the layout to circuit structure; estimate the area of the latch



homework

- 1-10 consider the design of a CMOS compound OR-AND-INVERT(OA21)gate computing $F = \overline{(A + B)C}$
 - Sketch a transistor-level schematic
 - Sketch a stick diagram
 - Estimate the area from the stick diagram
- 1-11 consider the design of a CMOS compound OR-AND-INVERT(OA22)gate computing $F = \overline{(A + B)(C + D)}$
 - Sketch a transistor-level schematic
 - Sketch a stick diagram
 - Estimate the area from the stick diagram