

Digital Integrated Circuits

A Design Perspective

Designing Combinational
Logic Circuits


Fuyuzhuo

School of Microelectronics, SJTU


homework

- Sketch a 4-input NAND gate with transistor widths chosen to achieve effective rise and fall resistance equal to a unit inverter.
 - Compute the rising and falling propagation delays(in terms of R and C) of the NAND gate driving h identical NAND gates using the ELMORE delay model
 - Compute the rising and falling contamination delays(in terms of R and C) of the NAND gate driving h identical NAND gates using the ELMORE delay model
 - If $C=2\text{fF}/\mu\text{m}$ and $R=2.5\text{kohm}\cdot\mu\text{m}$ in a 180nm, what is the delay of a fanout-of-3 NAND gate?

 
- Select gate sizes x and y for least delay from A to B



 - Consider four designs of a 6-input AND gate shown in figure. Develop an expression for delay of each path if the path electrical effort is H . What design is fastest for $H=1$? For $H=5$? For $H=20$? Explain your conclusion intuitively



- Consider a process in which pMOS transistors have three times the effective resistance as nMOS transistors. A unit inverter with equal rising and falling delays in this process is shown in figure. Calculate the logical efforts of a 2-input NAND gate and a 2-input NOR gate if they are designed with equal rising and falling delays
- Generalize the model if the pMOS transistors have u times the effective resistance of nMOS transistors. Find a general expression for the logical efforts of a k -input NAND gate and a k -input NOR gate. As u increases, comment on the relative desirability of NANDs vs. NORs.

 


Example, Revisited

- Ben Bitdiddle is the memory designer for the Motoroil 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.

- Decoder specifications:

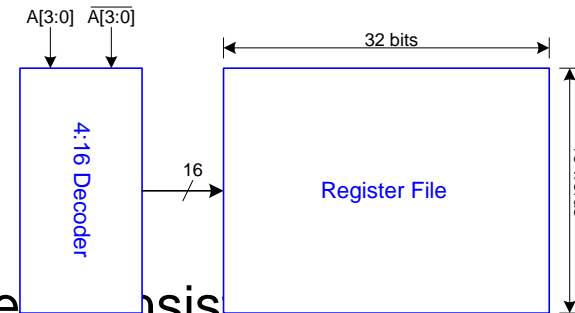- 16 word register file
- Each word is 64 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs $A[3:0]$
- Each input may drive 10 unit-sized transistors



- Ben needs to decide:
 - How many stages to use?
 - How large should each gate be?
 - How fast can decoder operate?

- Find the worst-case ELMORE parasitic delay of an n-input NOR gate

- Design a 4-input footed dynamic NAND gate driving an electrical effort of 1. estimate the worst charge sharing noise as a fraction of V_{dd} assuming that diffusion capacitance on uncontacted nodes is about half of gate capacitance and on contacted nodes it equals gate capacitance.

- Design a k-input AND gate with DeMorgan's law using static CMOS inverters followed by a k-input pseudo-nMOS NOR, as shown in figure. Let each inverter be unit-sized. If the output load is an inverter of size H, determine the best transistor sizes in the NOR gate and estimate the average delay of the path

