

Lecture 7. Element Stamping

Guoyong Shi, PhD

shiguoyong@ic.sjtu.edu.cn

School of Microelectronics

Shanghai Jiao Tong University

Spring 2010

Outline


- **Basic Concepts**
 - KVL/KCL
 - Circuit Element Equations
- **Sparse Tabular Analysis (STA)**
- **Nodal Analysis**
- **Modified Nodal Analysis (MNA)**

- **Part 1: Static Element Stamping**

Formulation of Circuit Equations

- **Kirchoff Current Law (KCL)**
- **Kirchoff Voltage Law (KVL)**
- **Circuit Element Equations**

Basic Concepts

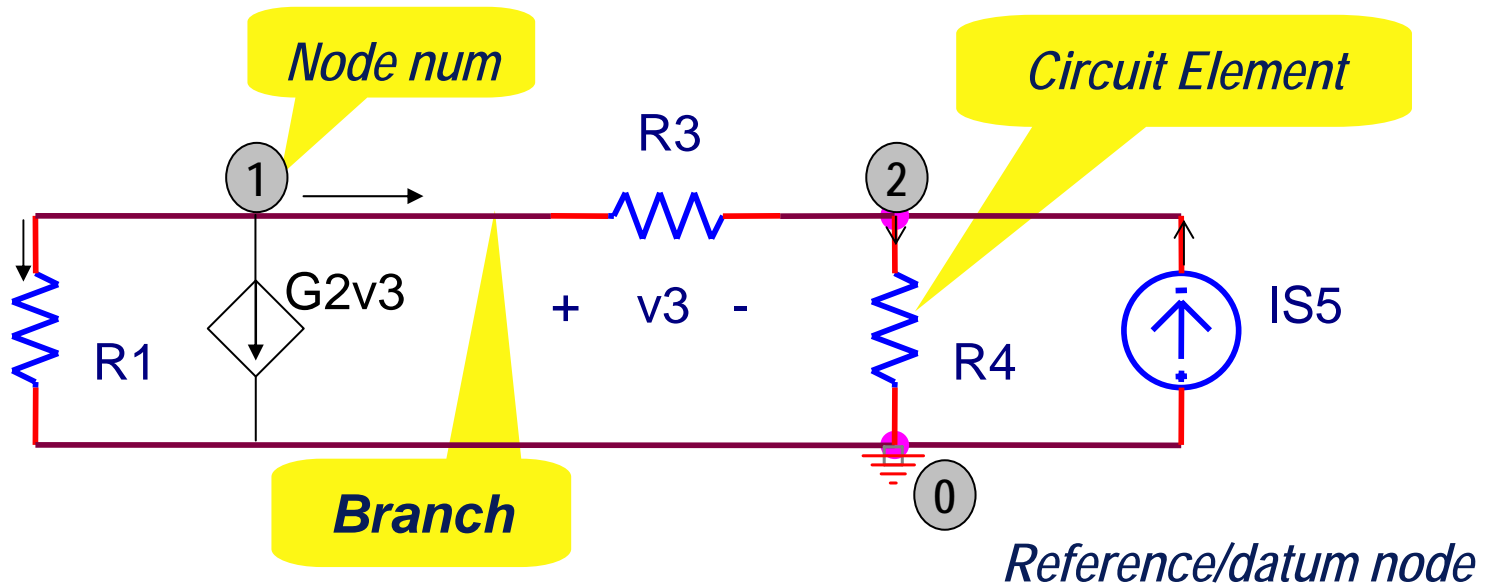


Basic Physical Quantities

KCL for nodes

KVL for loops

Node/Terminal Voltage e

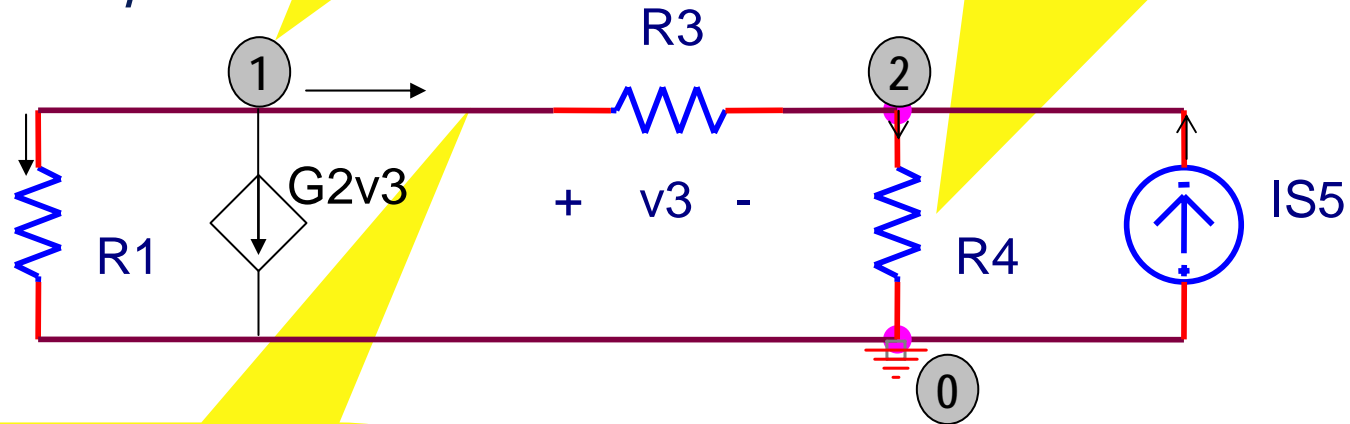Every circuit element (1 or 2 ports) is characterized by (i,v) equations



Branch current i
Branch voltage v

Reference node: $e = 0$

Circuit Element Equations


- **Mathematical models of circuit components are expressed in terms of ideal elements:**
 - Inductors
 - Capacitors
 - Resistors
 - Current Sources
 - Voltage Sources
 - Two Ports
 -
- **Physical quantities – current, voltage**
- **Some times, we need to use quantities: charge (nonlinear capacitor), flux (nonlinear inductor)**

Reference Directions

Two-terminal





Two-port


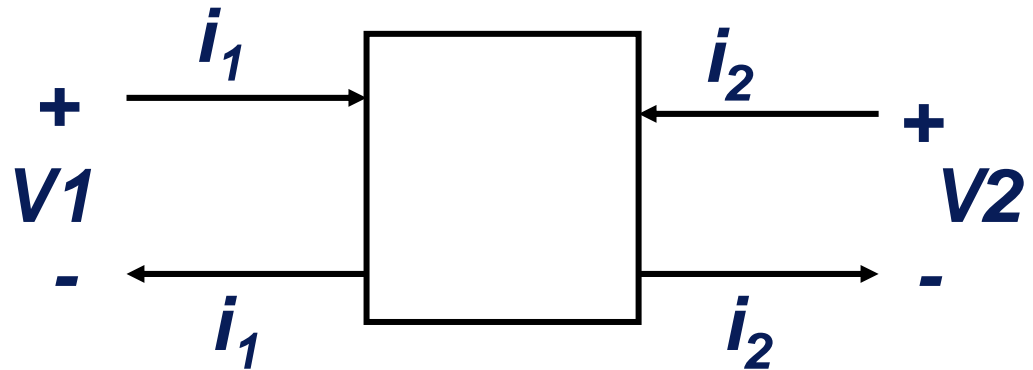


- *i and v are branch currents and voltages, respectively*
- *(Default) For each branch, current is directed from higher potential to lower potential*



Resistor

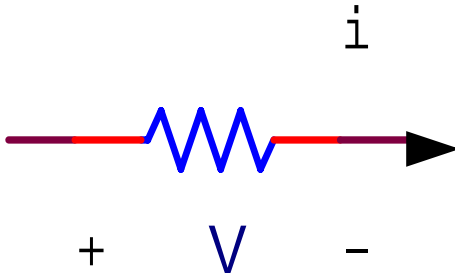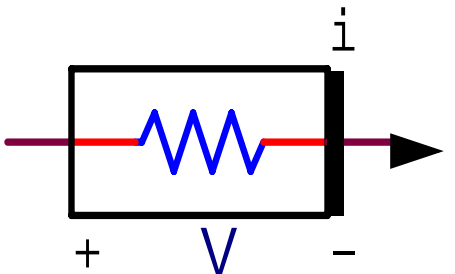Resistors	Symbol	Voltage controlled	Current controlled
Linear		$i = (1/R) v$	$v = R i$
Nonlinear		$i = i(v)$	$v = v(i)$



Capacitor

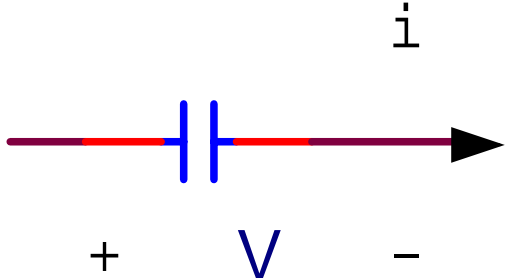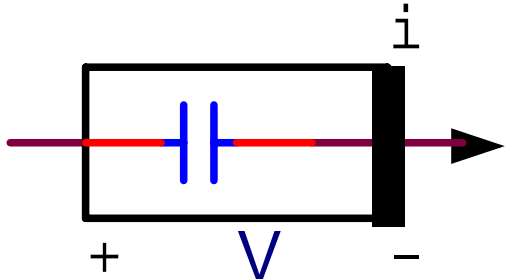Capacitor	Symbol	Voltage controlled
Linear		$q = C v$ $i = dq / dt$ Time-invariant C: $i = C dv/dt$
Nonlinear		$q = q (v)$ $i = dq / dt$ Time-invariant C: $i = C(v) dv/dt$


Two-Port Elements

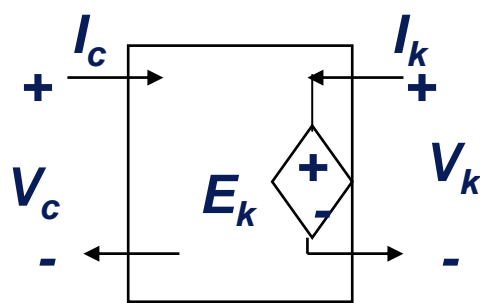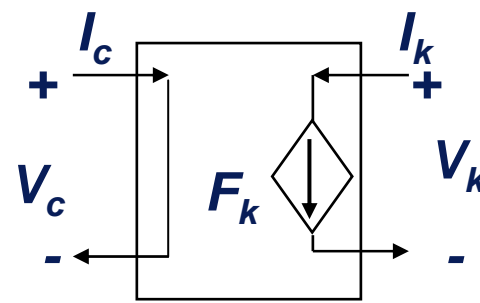Controlled Sources	Symbol	linear	Nonlinear
VCVS		$\mathbf{v}_k = \mathbf{E}_k \mathbf{v}_c$ $\mathbf{i}_c = \mathbf{0}$	$\mathbf{v}_k = \mathbf{v}_k(\mathbf{v}_c)$ $\mathbf{i}_c = \mathbf{0}$
CCCS		$\mathbf{i}_k = \mathbf{F}_k \mathbf{i}_c$ $\mathbf{v}_c = \mathbf{0}$	$\mathbf{i}_k = \mathbf{i}_k(\mathbf{i}_c)$ $\mathbf{v}_c = \mathbf{0}$

Topological Equations
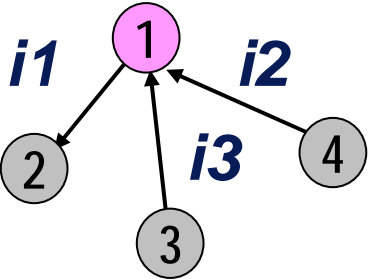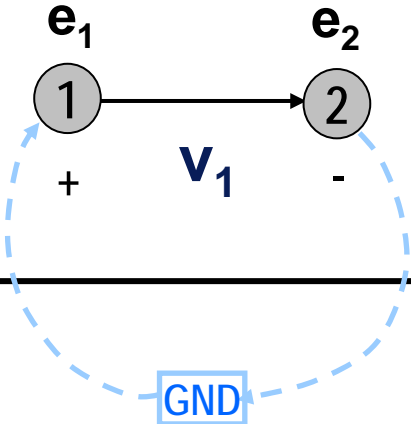
<p>KCL (branch currents) Current leaving a node is "+"</p>		<p>① $i_1 - i_2 - i_3 = 0$</p>
<p>KVL (nodal voltages) Voltage dropping is "+"</p>		$v_1 + e_2 - e_1 = 0$

Matrix Forms

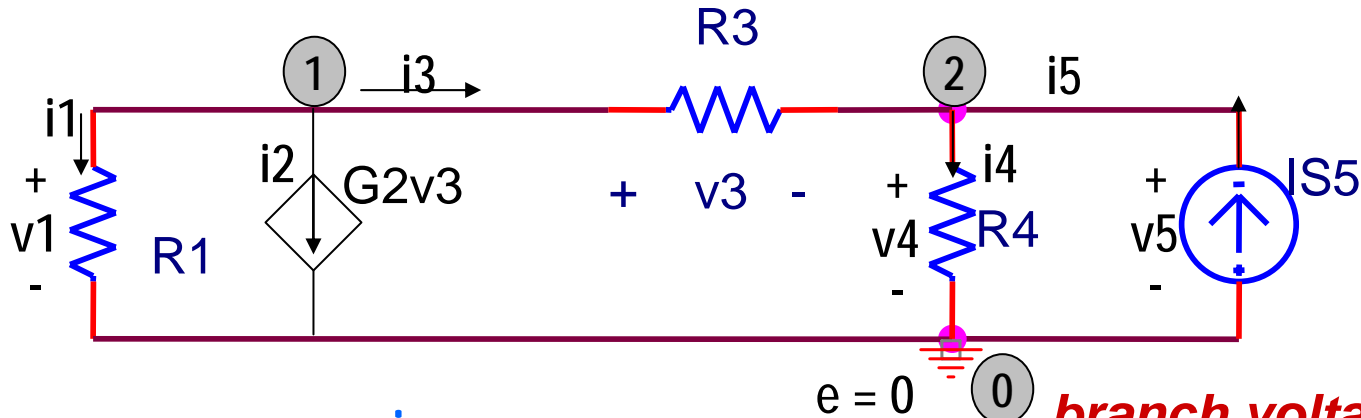

Nodal voltages

branch voltage vector

$$\begin{matrix} \textcircled{1} \\ \textcircled{2} \end{matrix} \begin{bmatrix} 1 & 1 & 1 & 0 & 0 \\ 0 & 0 & -1 & 1 & -1 \end{bmatrix} \begin{matrix} i \\ \downarrow \\ \begin{bmatrix} i1 \\ i2 \\ i3 \\ i4 \\ i5 \end{bmatrix} \end{matrix} = \begin{bmatrix} 0 \\ 0 \end{bmatrix}$$


$$\begin{bmatrix} v1 \\ v2 \\ v3 \\ v4 \\ v5 \end{bmatrix} - \begin{bmatrix} 1 & 0 \\ 1 & 0 \\ 1 & -1 \\ 0 & 1 \\ 0 & -1 \end{bmatrix} \begin{bmatrix} e1 \\ e2 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

KCL: $Ai = 0$

KVL $v - A^T e = 0$

**Tellegen's equation $i^T v = 0$
(conservation of energy)**

Incidence Matrix A

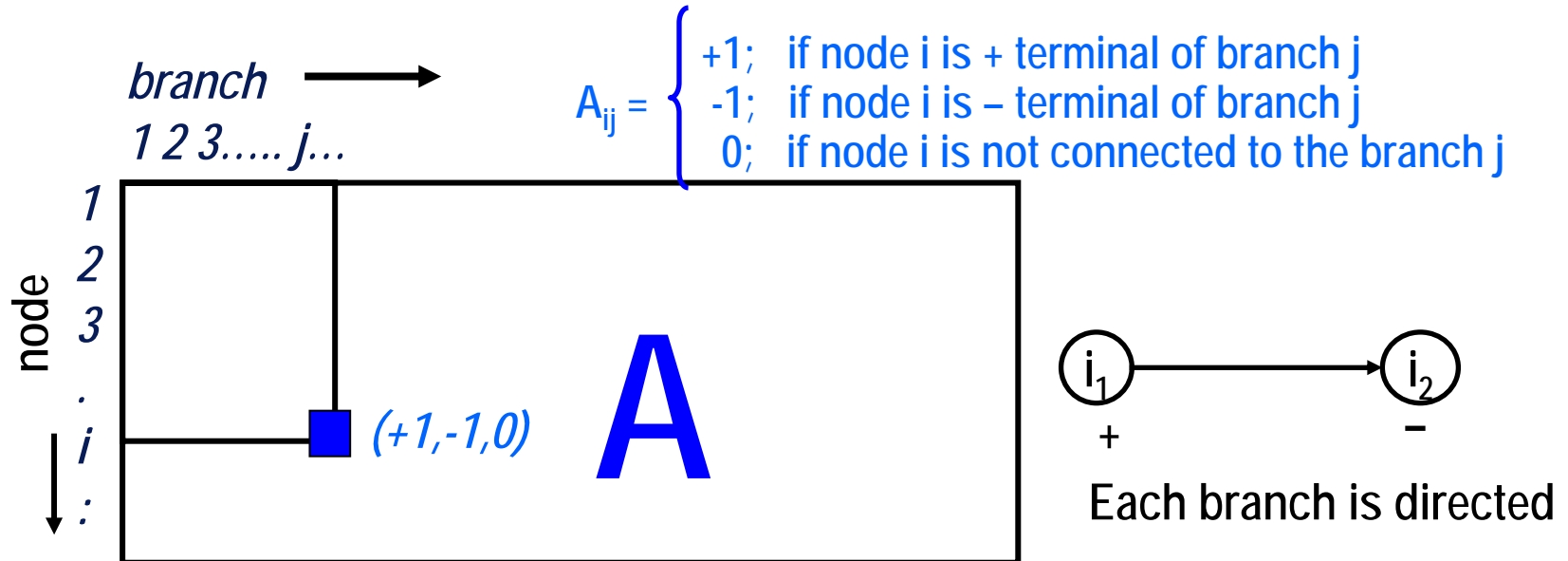

Properties

- A is **unimodular** (all minors equal to 1, -1, or 0)
- Only 2 nonzero entries in any column
- Sum of all rows of A is a zero vector.

Thus, pick a node as the reference (ground) node

Equation Assembly

- How does a computer assemble equations from the circuit description (netlist)?
- **Two systematic methods:**
 1. **Sparse Tableau Analysis (STA)**
Used by early ASTAP simulator (IBM)
 2. **Modified Nodal Analysis (MNA)**
Used by SPICE simulators

Sparse Tableau Analysis (STA)

Proposed by (Brayton, Gustavson, Hachtel 1969-71)

- Write KCL : $\mathbf{A}\mathbf{i} = \mathbf{0}$ n equations (one for each node)
- Write KVL : $\mathbf{v} - \mathbf{A}^T\mathbf{e} = \mathbf{0}$ b equations (one for each branch)
- Write Circuit Element (Branch) Equations :

$$\mathbf{K}_i\mathbf{i} + \mathbf{K}_v\mathbf{v} = \mathbf{S} \quad b \text{ equations}$$

*current
controlled*

*voltage
controlled*

sources

Sparse Tableau Analysis

Put all $(n + 2b)$ equations together:

$$\left[\begin{array}{ccc} \mathbf{A} & \mathbf{0} & \mathbf{0} \\ \mathbf{0} & \mathbf{I} & -\mathbf{A}^T \\ \mathbf{K}_i & \mathbf{K}_v & \mathbf{0} \end{array} \right] \left[\begin{array}{c} i \\ v \\ e \end{array} \right] = \left[\begin{array}{c} \mathbf{0} \\ \mathbf{0} \\ \mathbf{S} \end{array} \right]$$

*sparse
tableau*

$n + 2b$ unknowns

$n = \#nodes$

$b = \#branches$

Advantages of STA

- STA can be applied to any (linearized) circuit
- STA equations can be assembled directly from netlist
- STA coefficient matrix is **very sparse**

$$\begin{matrix}
 & \begin{matrix} \xrightarrow{2b} \\ \downarrow \end{matrix} & & \begin{matrix} \xrightarrow{2b} \\ \downarrow \end{matrix} & & & & \\
 \begin{matrix} b \\ \downarrow \\ \left(\begin{array}{cc|cc} A & 0 & 0 & 0 \\ 0 & I & -A^T & 0 \\ \hline K_i & K_v & & \end{array} \right) & \begin{pmatrix} i \\ v \\ e \end{pmatrix} & = & \begin{pmatrix} 0 \\ 0 \\ S \end{pmatrix} & & & & \\
 & & & & & & & \\
 & \begin{matrix} \xrightarrow{b} \\ \downarrow \end{matrix} & & & & & & \\
 & & & & & & & \\
 & \begin{matrix} \xrightarrow{b} \\ \downarrow \end{matrix} & & & & & &
 \end{matrix}
 \end{matrix}$$

$(2b+2b+b+b+b)$ nonzeros
 \therefore sparsity is $\frac{7b}{(n+2b)^2}$


Caution:

Sophisticated programming techniques and data structures are required for achieving the time and memory efficiency

Modified Nodal Analysis (MNA)

- A more compact formulation
- In MNA, every element is in **conductance** form!
- We'll review the steps how MNA is done.
- Introduced by McCalla, Nagel, Rohrer, Ruehli, Ho (1975)

Nodal Analysis

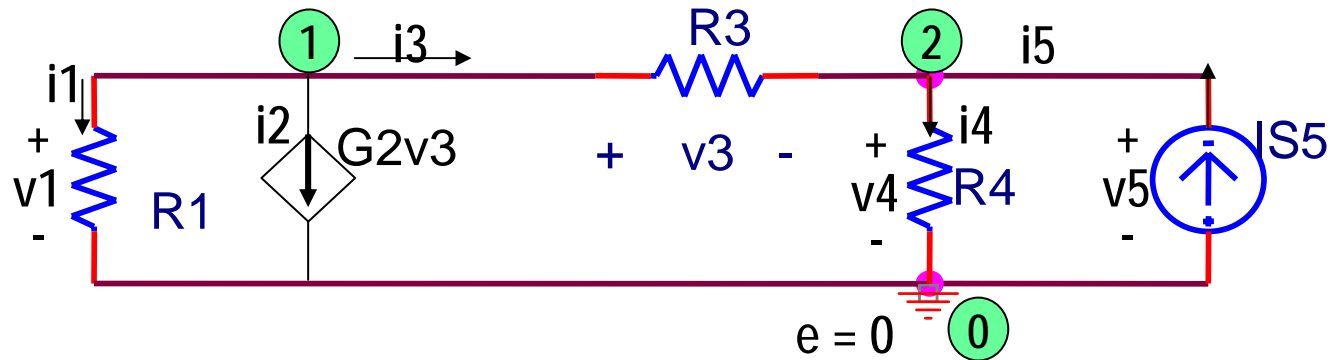

Step 1: Write KCL:

$$i_1 + i_2 + i_3 = 0 \quad (\text{node 1})$$

$$-i_3 + i_4 - i_5 = 0 \quad (\text{node 2})$$

Step 2: Substitute branch equations to rewrite KCL in branch voltages:

$$\frac{1}{R_1} v_1 + G_2 v_3 + \frac{1}{R_3} v_3 = 0 \quad (1)$$


$$-\frac{1}{R_3} v_3 + \frac{1}{R_4} v_4 = I_{S5} \quad (2)$$

Nodal Analysis

Step 3: Substitute branch voltages by nodal voltages (using KVL):

$$\frac{1}{R_1}e_1 + G_2(e_1 - e_2) + \frac{1}{R_3}(e_1 - e_2) = 0 \quad (1)$$
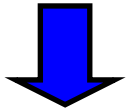
$$-\frac{1}{R_3}(e_1 - e_2) + \frac{1}{R_4}e_2 = I_{S5} \quad (2)$$




Put in matrix form

$$\begin{bmatrix} \frac{1}{R_1} + G_2 + \frac{1}{R_3} & -G_2 - \frac{1}{R_3} \\ -\frac{1}{R_3} & \frac{1}{R_4} + \frac{1}{R_3} \end{bmatrix} \begin{pmatrix} e_1 \\ e_2 \end{pmatrix} = \begin{pmatrix} 0 \\ I_{S5} \end{pmatrix}$$

$$Y_n e = S$$

Red arrows point from the matrix Y_n , the vector e , and the vector S in the matrix equation above to the corresponding terms in this simplified equation.

Regularity in MNA Matrix

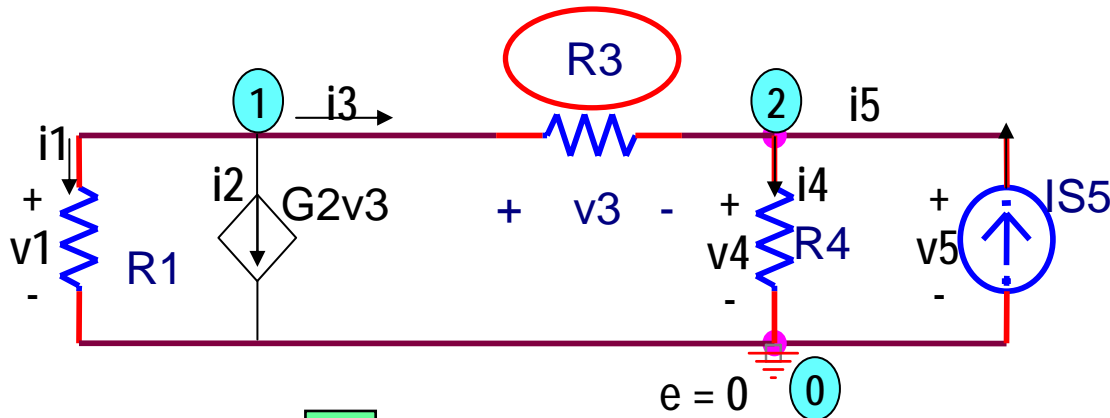

↓ Stamping

$$\begin{matrix}
 \textcircled{1} \\
 \textcircled{2}
 \end{matrix}
 \begin{bmatrix}
 \textcircled{1} & \textcircled{2} \\
 \textcircled{1} & \textcircled{2}
 \end{bmatrix}
 \begin{bmatrix}
 \frac{1}{R_1} + G_2 + \frac{1}{R_3} & -G_2 - \frac{1}{R_3} \\
 -\frac{1}{R_3} & \frac{1}{R_4} + \frac{1}{R_3}
 \end{bmatrix}$$


↖ Coefficient matrix

- Each element contributes (in **conductance form**) only to the entries with row-column positions corresponding to the node numbers.
- Such a regular format is called a “**stamp**”

Resistor Stamp

SPICE Netlist Format (R)

R_k N_+ N_- $value_of_R_k$

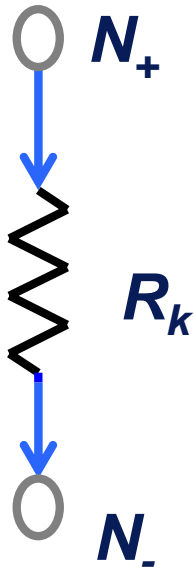


	N_+		N_-	
	\vdots		\vdots	
$N_+ \dots$	$\frac{1}{R_k}$	\dots	$-\frac{1}{R_k}$	\dots
	\vdots		\vdots	
$N_- \dots$	$-\frac{1}{R_k}$	\dots	$\frac{1}{R_k}$	\dots
	\vdots		\vdots	

VCCS Stamp

SPICE Netlist Format (VCCS)

G_k N_+ N_- NC_+ NC_- $value_of_G_k$

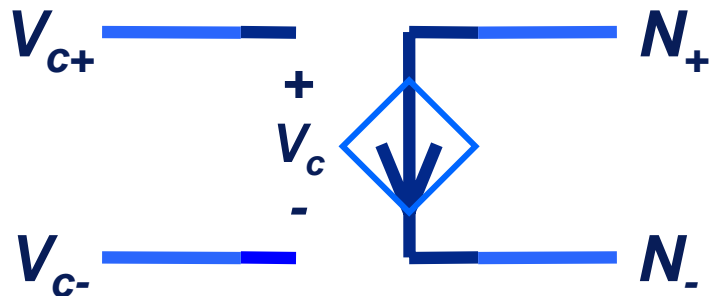Similar to a resistor; but note that the row/col indices are different.



			NC_+		NC_-	
			⋮		⋮	
N_+	⋯	G_k	⋯	$-G_k$	⋯	
		⋮		⋮		
N_-	⋯	$-G_k$	⋯	G_k	⋯	
		⋮		⋮		

Current Source Stamp

SPICE Netlist Format (Current Source)


ISK N+ N- value_of_I_k

Note the signs in this case!

$$\begin{pmatrix} \vdots \\ -I_k \\ \vdots \\ +I_k \\ \vdots \end{pmatrix}$$

N+


N-

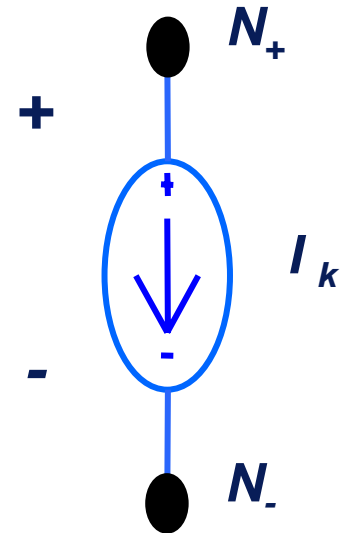


Right-Hand Side (RHS)

Relation between STA and NA

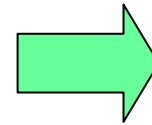
$$K_i^{-1} \rightarrow \begin{pmatrix} K_i & -K_v & 0 \\ 0 & I & -A^T \\ A & 0 & 0 \end{pmatrix} \begin{pmatrix} i \\ v \\ e \end{pmatrix} = \begin{pmatrix} S \\ 0 \\ 0 \end{pmatrix}$$


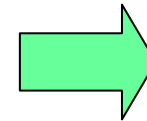
$$-A \begin{pmatrix} I & -K_i^{-1}K_v & 0 \\ 0 & I & -A^T \\ A & 0 & 0 \end{pmatrix} \begin{pmatrix} i \\ v \\ e \end{pmatrix} = \begin{pmatrix} K_i^{-1}S \\ 0 \\ 0 \end{pmatrix}$$


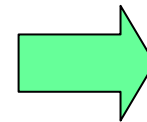
$$\begin{pmatrix} I & -K_i^{-1}K_v & 0 \\ 0 & I & -A^T \\ 0 & AK_i^{-1}K_v & 0 \end{pmatrix} \begin{pmatrix} i \\ v \\ e \end{pmatrix} = \begin{pmatrix} K_i^{-1}S \\ 0 \\ -AK_i^{-1}S \end{pmatrix}$$



Relation between STA and NA

$$\begin{array}{c} -AK_i^{-1}K_v \\ \downarrow \end{array} \begin{pmatrix} I & -K_i^{-1}K_v & 0 \\ 0 & I & -A^T \\ 0 & AK_i^{-1}K_v & 0 \end{pmatrix} \begin{pmatrix} i \\ v \\ e \end{pmatrix} = \begin{pmatrix} K_i^{-1}S \\ 0 \\ -AK_i^{-1}S \end{pmatrix} \quad \rightarrow$$

Tableau Matrix

$$\begin{array}{c} \rightarrow \end{array} \begin{pmatrix} I & -K_i^{-1}K_v & 0 \\ 0 & I & -A^T \\ 0 & 0 & AK_i^{-1}K_v A^T \end{pmatrix} \begin{pmatrix} i \\ v \\ e \end{pmatrix} = \begin{pmatrix} K_i^{-1}S \\ 0 \\ -AK_i^{-1}S \end{pmatrix}$$

Y_n
 Is

MNA

$Y_n e = Is$

After solving e , we get v , then get i .

Nodal Analysis -- Advantages & Problem

- Advantages:


- Circuit equations can be assembled by stamping
- Yn is sparse (but not as sparse as STA) and small ($n \times n$), smaller than STA ($n + 2b \times n + 2b$)
- Yn has non-zero diagonal entries and is often diagonally dominant

- Problem:


Nodal Analysis cannot handle the following

- Floating independent voltage source (not connected to ground)
- **VCVS** (E-ELEMENT)
- **CCCS** (F-ELEMENT)
- (VCCS ok!) (G-ELEMENT)
- **CCVS** (H-ELEMENT)

Modified Nodal Analysis (MNA)

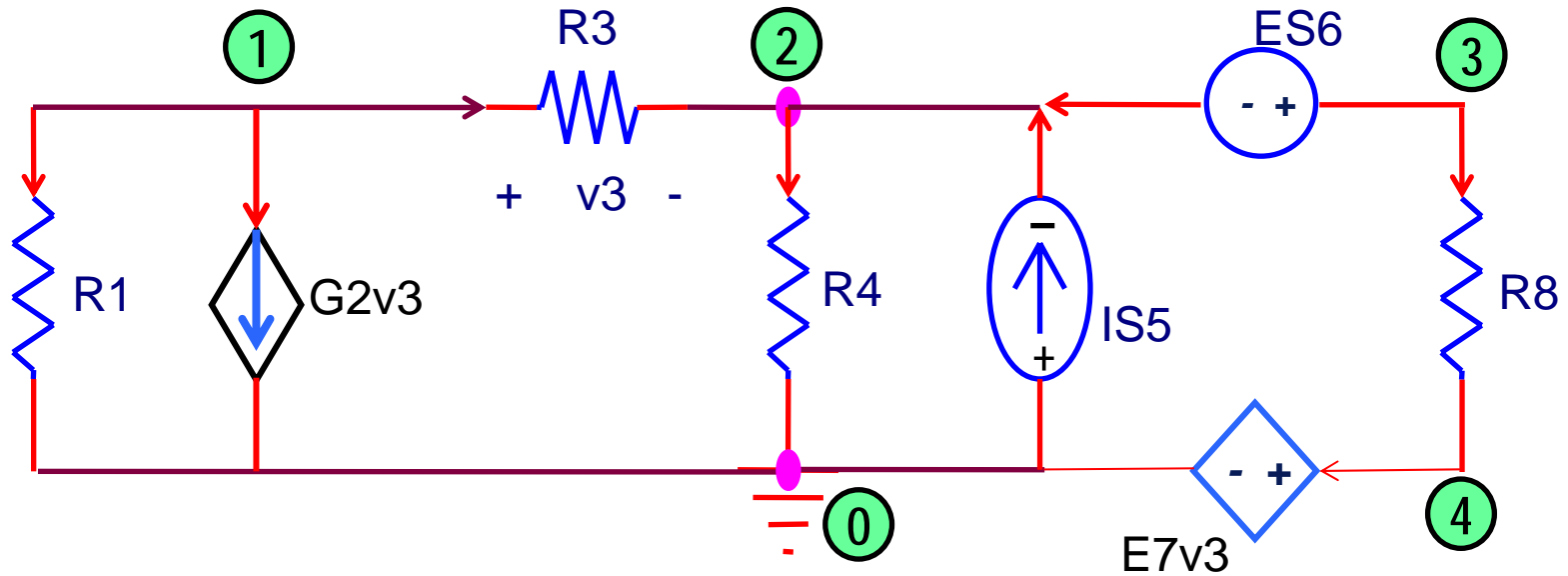

Modified Nodal Analysis (MNA)

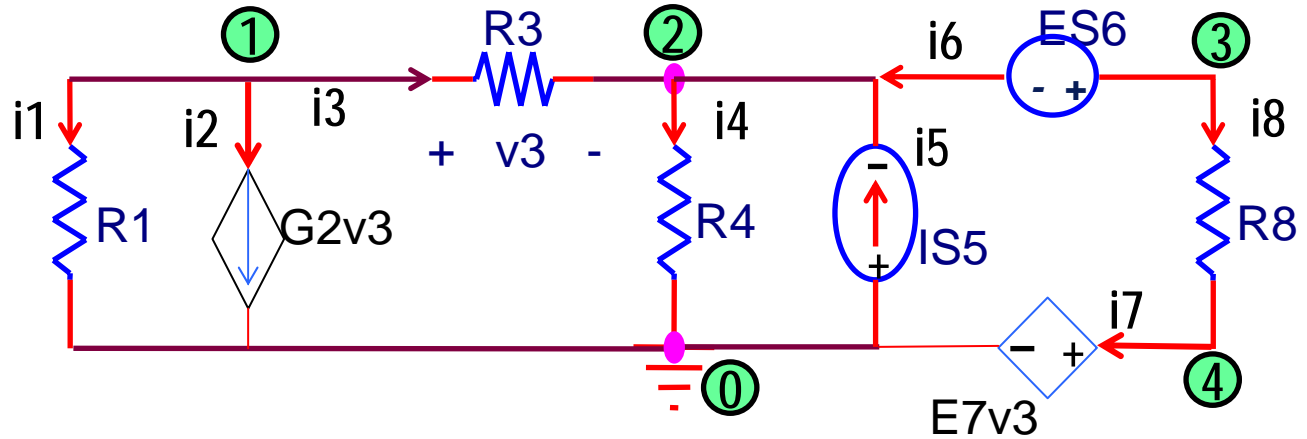

Step 1: Write KCL

$$i1 + i2 + i3 = 0 \quad (1)$$

$$-i3 + i4 - i5 - i6 = 0 \quad (2)$$

$$i6 + i8 = 0 \quad (3)$$

$$i7 - i8 = 0 \quad (4)$$

Modified Nodal Analysis (MNA)

Step 2: Substitute branch currents by branch voltages

$$\frac{1}{R1}v1 + G2v3 + \frac{1}{R3}v3 = 0 \quad (1)$$

$$-\frac{1}{R3}v3 + \frac{1}{R4}v4 - i6 = IS5 \quad (2)$$

$$i6 + \frac{1}{R8}v8 = 0 \quad (3)$$


$$i7 - \frac{1}{R8}v8 = 0 \quad (4)$$

Modified Nodal Analysis (MNA)

Step 3: Write down unused branch equations

$$v_6 = ES_6 \quad (4)$$

$$v_7 - E_7 v_3 = 0 \quad (5)$$

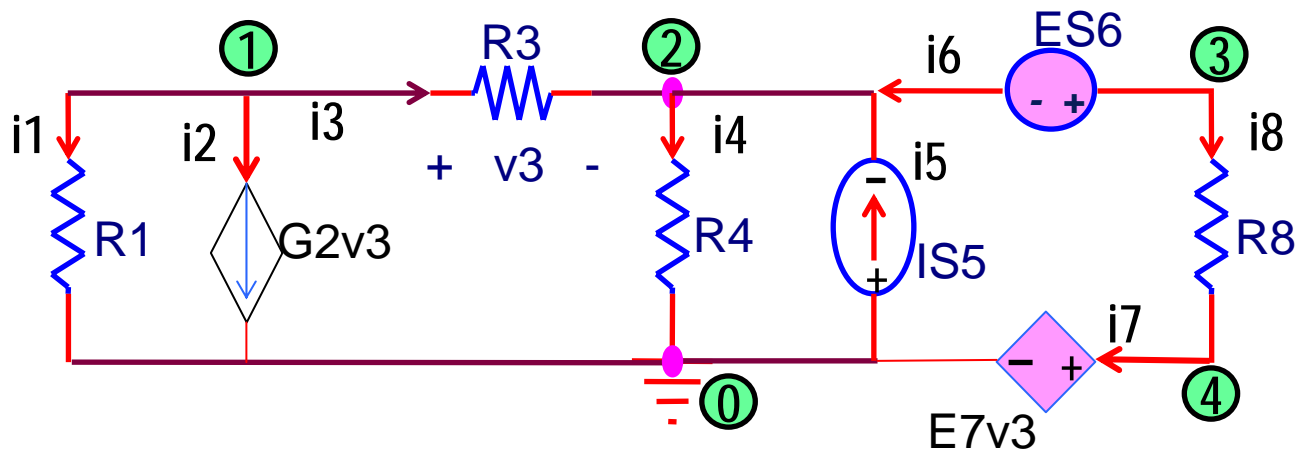

Modified Nodal Analysis (MNA)

Step 4: Substitute branch voltages by nodal voltages

$$\frac{1}{R1}e1 + G2(e1 - e2) + \frac{1}{R3}(e1 - e2) = 0 \quad (1)$$

$$-\frac{1}{R3}(e1 - e2) + \frac{1}{R4}e2 - i6 = IS5 \quad (2)$$

$$i6 + \frac{1}{R8}(e3 - e4) = 0 \quad (3)$$

$$i7 - \frac{1}{R8}(e3 - e4) = 0 \quad (4)$$

$$(e3 - e2) = ES6 \quad (5)$$

$$e4 - E7(e1 - e2) = 0 \quad (6)$$

Modified Nodal Analysis (MNA)

$$\begin{array}{l}
 \text{node-1} \rightarrow \\
 \text{node-2} \rightarrow \\
 \text{node-3} \rightarrow \\
 \text{node-4} \rightarrow \\
 \text{branch-6} \rightarrow \\
 \text{branch-7} \rightarrow
 \end{array}
 \begin{bmatrix}
 \frac{1}{R1} + G2 + \frac{1}{R3} & -G2 & 0 & 0 & 0 & 0 \\
 -\frac{1}{R3} & \frac{1}{R3} + \frac{1}{R4} & 0 & 0 & -1 & 0 \\
 0 & 0 & \frac{1}{R8} & -\frac{1}{R8} & 1 & 0 \\
 0 & 0 & -\frac{1}{R8} & \frac{1}{R8} & 0 & 1 \\
 0 & -1 & 1 & 0 & 0 & 0 \\
 E7 & -E7 & 0 & -1 & 0 & 0
 \end{bmatrix}
 \begin{bmatrix}
 e1 \\
 e2 \\
 e3 \\
 e4 \\
 i6 \\
 i7
 \end{bmatrix}
 =
 \begin{bmatrix}
 0 \\
 IS5 \\
 0 \\
 0 \\
 ES6 \\
 0
 \end{bmatrix}$$

node-1, node-2, node-3, node-4, branch-6, branch-7 labels are on the left.

 node-1, node-2, node-3, node-4 labels are below the matrix.

 branch-6, branch-7 labels are to the right of the matrix.


 node voltages label is below the matrix.

 some branch currents label is below the matrix.

$$\begin{pmatrix} Y_n & B \\ C & 0 \end{pmatrix}
 \begin{pmatrix} e \\ i \end{pmatrix}
 = RHS$$

node voltages label points to the e vector.

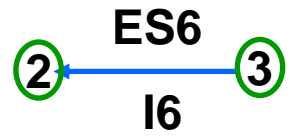
 some branch currents label points to the i vector.



Voltage Source Stamp

SPICE Netlist Format (Floating voltage source)

V_k N+ N- value_of_Vk

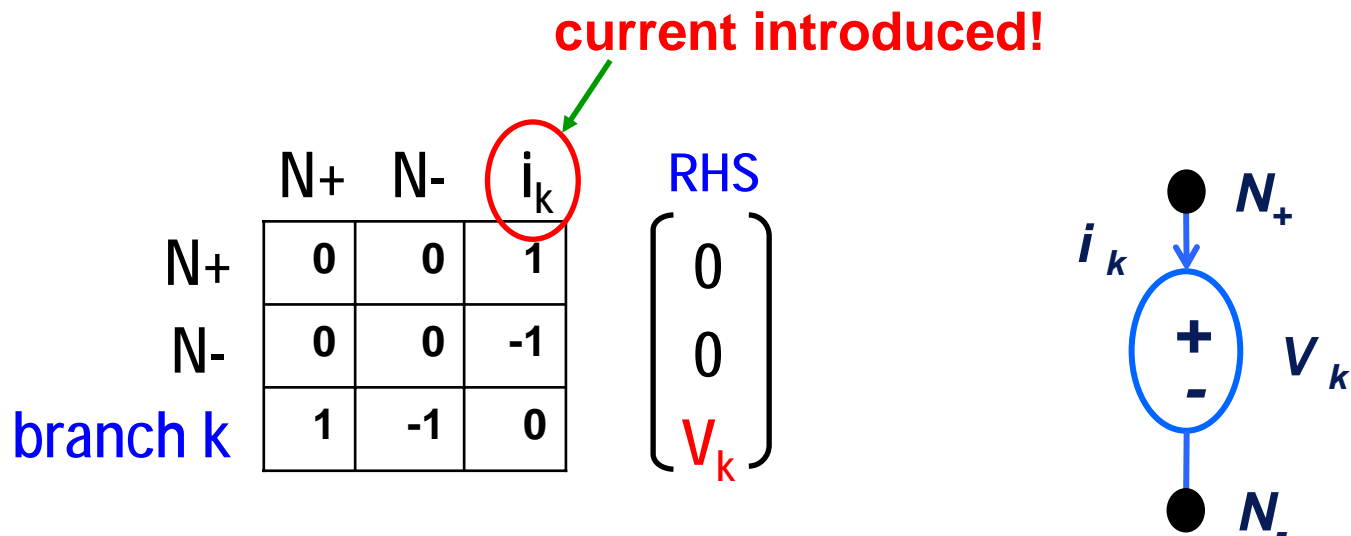


CCCS Stamp

SPICE Netlist Format (CCCS)

F_k $N+$ $N-$ $Vname$ $value_of_F_k$
 $Vname$ $NC+$ $NC-$ $value$

	N_+	N_-	NC_+	NC_-	i_c	RHS
N_+					F_k	0
N_-					$-F_k$	0
NC_+					1	0
NC_-					-1	0
br V_c			1	-1		V_c

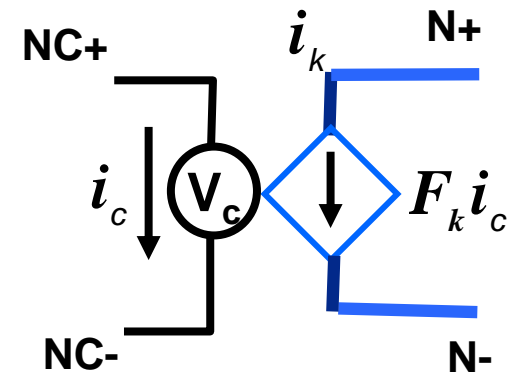


* If 'Vname' is used as a CC for multiple times, it is stamped **only once** though!

CCVS Stamp

SPICE Netlist Format (CCVS)

H_k $N+$ $N-$ $Vname$ $value_of_H_k$
 $Vname$ $NC+$ $NC-$ $value$

	N_+	N_-	NC_+	NC_-	i_k	i_c	RHS
N_+					1		0
N_-					-1		0
NC_+						1	0
NC_-						-1	0
br-k	1	-1				$-H_k$	0
br-c			1	-1			V_c

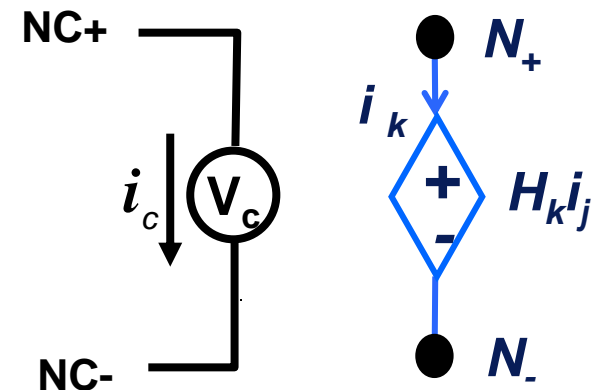


* If 'Vname' is used as a CC for multiple times, it is stamped **only once** though!

VCVS Stamp

SPICE Netlist Format (VCVS)

E_k N_+ N_- NC_+ NC_- value_of_ E_k

	N_+	N_-	NC_+	NC_-	i_k
N_+					1
N_-					-1
NC_+					
NC_-					
br k	1	-1	$-E_k$	E_k	

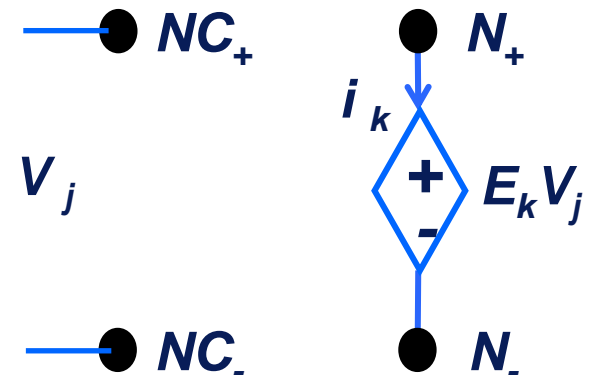

General Rules for MNA

- A branch current is introduced as an additional variable for a **voltage source** or an **inductor**
- For current sources, resistors, conductance and capacitors, the branch current is introduced only if
 - Any circuit element depends on that branch current; or
 - The branch current is requested as an output.

Modified Nodal Analysis (MNA)

Advantages of MNA

- **MNA can be applied to any circuit**
- **MNA equations can be assembled “directly” from a circuit description (e.g. netlist)**

Problem

- **Sometimes zeros appear on the main diagonal; causing some principle minors to be singular (numerical instability.)**

Summary

- KVL/KCL + Circuit Element Equations
- Equations formulation: STA and MNA
- MNA was implemented in most simulators (SPICE)
- Element stamps
- **A key observation:**
 - **Circuit matrix structure will not change!** (exploited by SPICE for speedup – **symbolic factorization**)

Assignment 3

- **Implement a netlist parser that reads a simple netlist with the following elements**
 - R
 - Vsource, Isource
 - VCVS, CCCS, VCCS, CCVS

Print the stamps and the RHS with row and column indices.

Part 2.
Dynamic Element Stamping

Outline

- **Discretization Formulas for d/dt**
- **Element Stamps for Linear Capacitors and Inductors**



Circuit with dynamic element

$$RC \frac{dV_c}{dt} + V_c = V_s, \quad V_c(0) = 0$$



Analytical solution
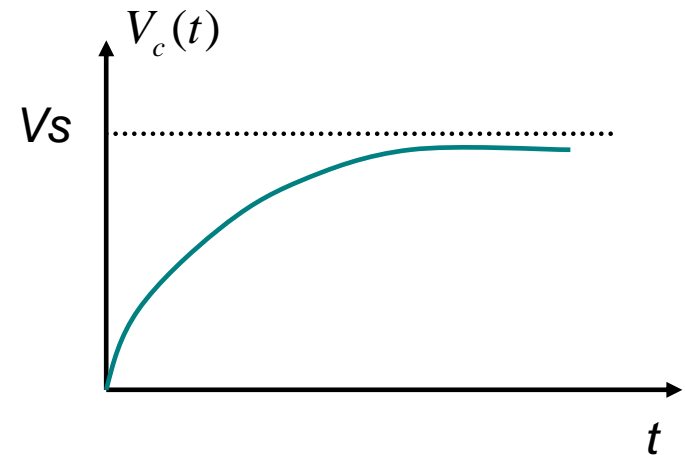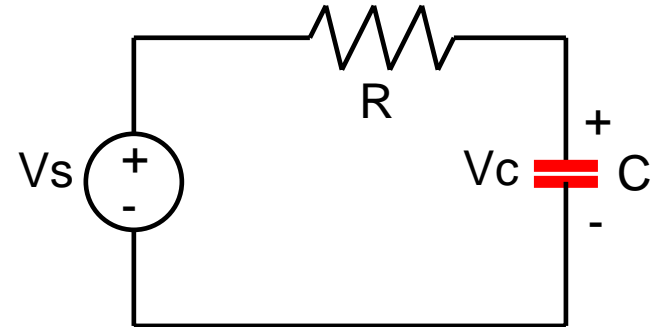
$$V_c(t) = V_s \left(1 - e^{-\frac{t}{\tau}} \right), \quad \tau = RC$$



- How to solve it numerically?

Numerical Solution

$$\frac{dV}{dt} + V = V_s, \quad V(0) = 0$$

Assuming $\tau = RC = 1$

- Replace the derivative by difference

$$\frac{V(t+h) - V(t)}{h} + V(t) = V_s$$

$h = \text{time step (small)}$


There are many ways to do discretization.

$$V(t+h) = V(t) + h[V_s - V(t)]$$

← Becomes iteration

Forward Euler (FE)
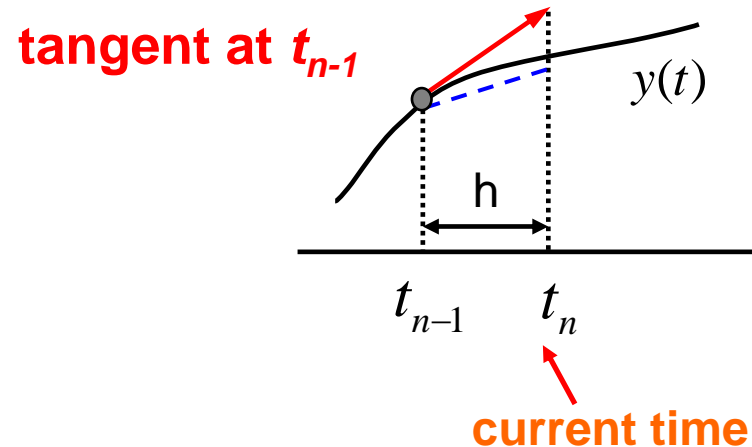
$$\dot{y}(t) = \frac{dy(t)}{dt} = f(y(t))$$




$$\frac{y(t_n) - y(t_{n-1})}{h} \approx \dot{y}(t_{n-1}) = f(y(t_{n-1}))$$

$$y(t_n) = y(t_{n-1}) + h \cdot f(y(t_{n-1}))$$

Direct iteration; (no linear / nonlinear solve involved)

Backward Euler (BE)
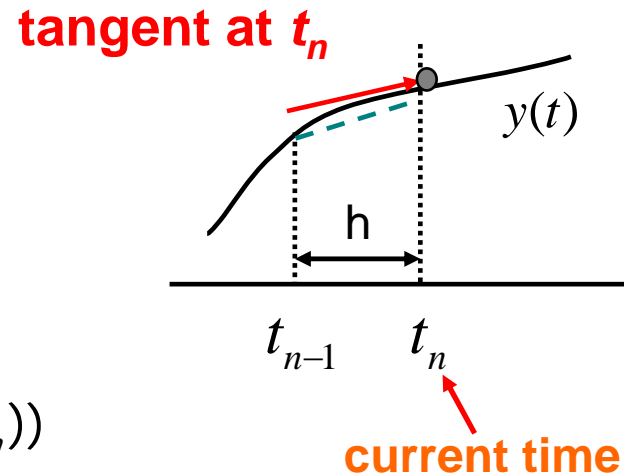
$$\dot{y}(t) = \frac{dy(t)}{dt} = f(y(t))$$



$$\frac{y(t_n) - y(t_{n-1})}{h} \approx \dot{y}(t_n) = f(y(t_n))$$

$$y(t_n) = y(t_{n-1}) + h \cdot f(y(t_n))$$

$y(t_n)$ appears on both sides of the equation; need to solve $y(t_n)$ by iterations if $f(\cdot)$ is nonlinear.

FE and BE

Forward Euler:

$$y(t_n) = y(t_{n-1}) + h \cdot f(y(t_{n-1}))$$

Backward Euler:


$$y(t_n) = y(t_{n-1}) + h \cdot f(y(t_n))$$

- Although B.E. requires more computation, it is preferred in practice because it is more numerically stable.
- Will discuss on this later.

Trapezoidal Rule (TR)

$$\dot{y}(t) = \frac{dy(t)}{dt} = f(y(t))$$

tangents at both t_{n-1} and t_n

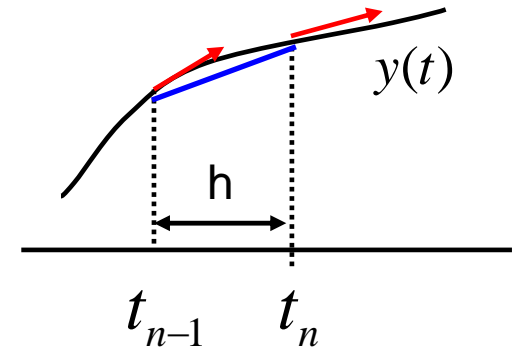

$$\frac{y(t_n) - y(t_{n-1})}{h} \approx \frac{1}{2} [\dot{y}(t_n) + \dot{y}(t_{n-1})]$$

slope of secant

averaged tangent

$$\frac{y(t_n) - y(t_{n-1})}{h} \approx \frac{1}{2} [f(y(t_n)) + f(y(t_{n-1}))]$$

$$y(t_n) = y(t_{n-1}) + \frac{h}{2} [f(y(t_n)) + f(y(t_{n-1}))]$$

Again, requires solving $y(t_n)$ from a set of nonlinear equations

FE, BE and TR

$$\dot{y}(t) = \frac{dy(t)}{dt} = f(y(t))$$

Forward Euler:

$$y(t_n) = y(t_{n-1}) + h \cdot f(y(t_{n-1}))$$

Backward Euler:

$$y(t_n) = y(t_{n-1}) + h \cdot f(y(t_n))$$

Trapezoidal Rule:

$$y(t_n) = y(t_{n-1}) + \frac{h}{2} [f(y(t_n)) + f(y(t_{n-1}))]$$

- **Trapezoidal rule has even better numerical property than B.E.**

Interpretation of Trapezoidal Rule



- Trapezoidal rule comes from numerical integration – computing the area under a curve

$$\dot{x}(t) = g(t)$$

$$x(t_n) = x(t_{n-1}) + \int_{t_{n-1}}^{t_n} g(\tau) d\tau$$

$$x(t_n) \approx x(t_{n-1}) + \frac{h}{2} [g(t_n) + g(t_{n-1})]$$

approximated by a trapezoidal

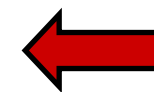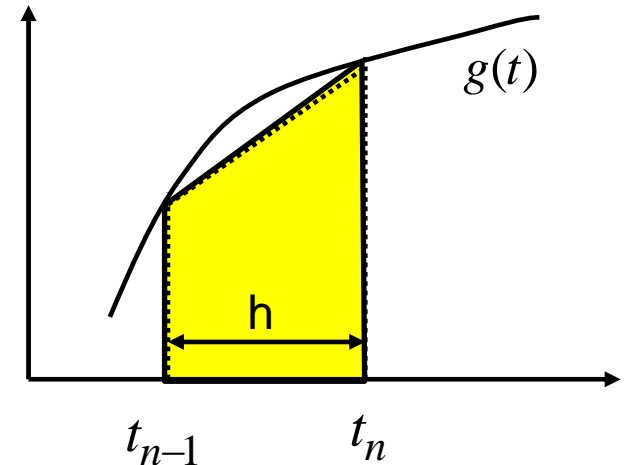

Trapezoidal Rule

$$\frac{x(t_n) - x(t_{n-1})}{h} \approx \frac{1}{2} [\dot{x}(t_n) + \dot{x}(t_{n-1})]$$

Stamps of Dynamic Elements


- **Stamps for dynamic elements can be derived from a discretization method:**
 - Capacitor (C)
 - Inductor (L)
 - Others ...

Capacitor Stamp

$$i(t) = C \frac{dv(t)}{dt}$$



discretized by B.E.

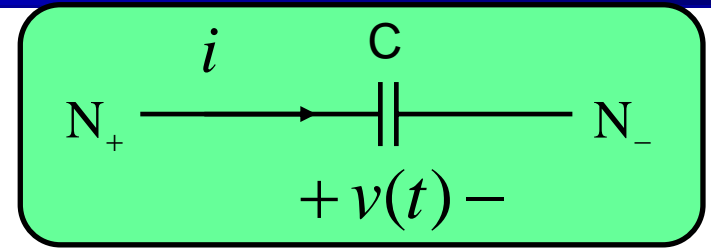

$$i(t) = \frac{C}{h} [v(t) - v(t-h)] = \frac{C}{h} v(t) - \frac{C}{h} v(t-h)$$

NA Stamp

	N_+	N_-	RHS
N_+	$\frac{C}{h}$	$-\frac{C}{h}$	$\frac{C}{h} v(t-h)$
N_-	$-\frac{C}{h}$	$\frac{C}{h}$	$-\frac{C}{h} v(t-h)$

MNA Stamp

treated as source

branch C


	N_+	N_-	i	RHS
N_+			1	0
N_-			-1	0
branch C	$\frac{C}{h}$	$-\frac{C}{h}$	-1	$\frac{C}{h} v(t-h)$

$$\frac{C}{h} v(t) - i(t) = \frac{C}{h} v(t-h)$$


Inductor Stamp

discretized by B.E.
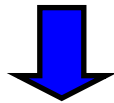
$$v(t) = L \frac{di}{dt} \approx L \frac{i(t) - i(t-h)}{h}$$


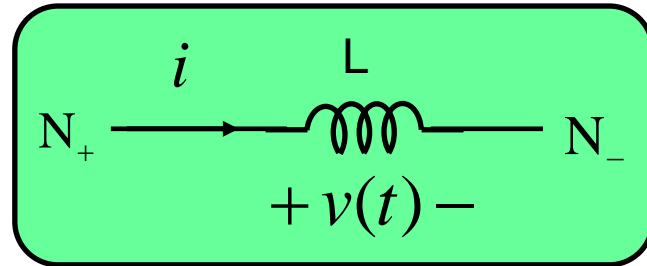
$$v(t) - \frac{L}{h} i(t) = -\frac{L}{h} i(t-h)$$



branch L

	N_+	N_-	i	RHS
N_+			1	0
N_-			-1	0
branch L	1	-1	$-\frac{L}{h}$	$-\frac{L}{h} i(t-h)$

(must introduce current)

MNA Stamp

Stamps for C & L

NA Stamp for C

$$\begin{array}{c} N_+ \\ N_- \end{array} \left[\begin{array}{cc|c} N_+ & N_- & \text{RHS} \\ \hline \frac{C}{h} & -\frac{C}{h} & \frac{C}{h}v(t-h) \\ -\frac{C}{h} & \frac{C}{h} & -\frac{C}{h}v(t-h) \end{array} \right]$$

MNA Stamp for C


$$\begin{array}{c} N_+ \\ N_- \end{array} \left[\begin{array}{ccc|c} N_+ & N_- & i & \text{RHS} \\ \hline & & 1 & 0 \\ & & -1 & 0 \\ \frac{C}{h} & -\frac{C}{h} & -1 & \frac{C}{h}v(t-h) \end{array} \right]$$

MNA Stamp for L

$$\begin{array}{c} N_+ \\ N_- \end{array} \left[\begin{array}{ccc|c} N_+ & N_- & i & \text{RHS} \\ \hline & & 1 & 0 \\ & & -1 & 0 \\ 1 & -1 & -\frac{L}{h} & -\frac{L}{h}i(t-h) \end{array} \right]$$

Note that: Stamps for C or L depend on the discretization method used!

A Circuit Example

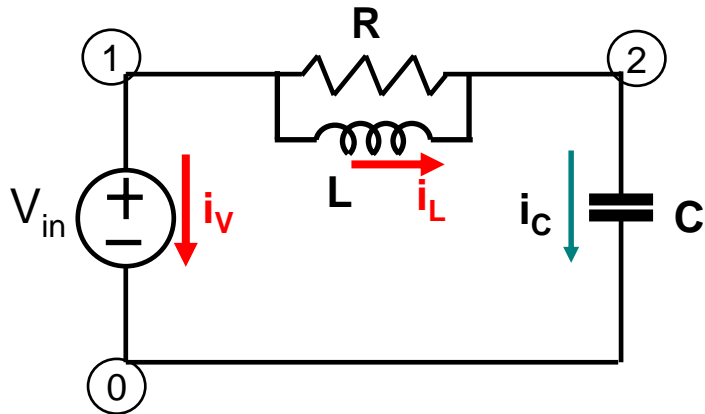

$$v_L(t) = L \frac{di_L(t)}{dt}$$

$$v_1(t) - v_2(t) = \frac{L}{h} [i_L(t) - i_L(t-1)]$$

branch L

branch V_{in}

$$i_c(t) = \frac{C}{h} [v_C(t) - v_C(t-1)]$$

$$= \frac{C}{h} [v_2(t) - v_0(t)] - = \frac{C}{h} [v_2(t-1) - v_0(t-1)]$$

	0	1	2	3	4	RHS
0	$\frac{C}{h}$	0	$-\frac{C}{h}$	0	-1	$-\frac{C}{h} v_C(t-h)$
1	0	$\frac{1}{R}$	$-\frac{1}{R}$	1	1	0
2	$-\frac{C}{h}$	$-\frac{1}{R}$	$(\frac{1}{R} + \frac{C}{h})$	-1		$\frac{C}{h} v_C(t-h)$
3	0	1	-1	$-\frac{L}{h}$		$-\frac{L}{h} i_L(t-h)$
4	-1	1				V_{in}

Assignment 4

- **Derive the stamps for C and L using the Trapezoidal Rule (both in MNA).**

Classical Papers

1. G.D. Hachtel, R.K. Brayton and F.G. Gustavson, “**The sparse tableau approach to network analysis and design**,” *IEEE Trans. Circuit Theory*, vol.CT-18, Jan. **1971**, pp. 101-119.
2. C.W. Ho, A.E. Ruehli and P.A. Brennan, “**The modified nodal approach to network analysis**”, *IEEE Trans. Circuits and Systems*, CAS-22, June **1975**, pp. 504-509