



Introduction to CMOS RF Integrated Circuits Design

VI. Phase-Locked Loops



Outline

- Introduction
- Basic Feedback Loop Theory
- Circuit Implementation


What is a PLL?

- A PLL is a negative feedback system where an oscillator-generated signal is phase and frequency locked to a reference signal.

Can be used as:

- Frequency Synthesis (e.g. generating a 1 GHz clock from a 100 MHz reference)
- Skew Cancellation (e.g. phase-aligning an internal clock to the IO clock) (May use a DLL instead)
- Extracting a clock from a random data stream (e.g. serial-link receiver)

Charge-Pump PLL Block Diagram

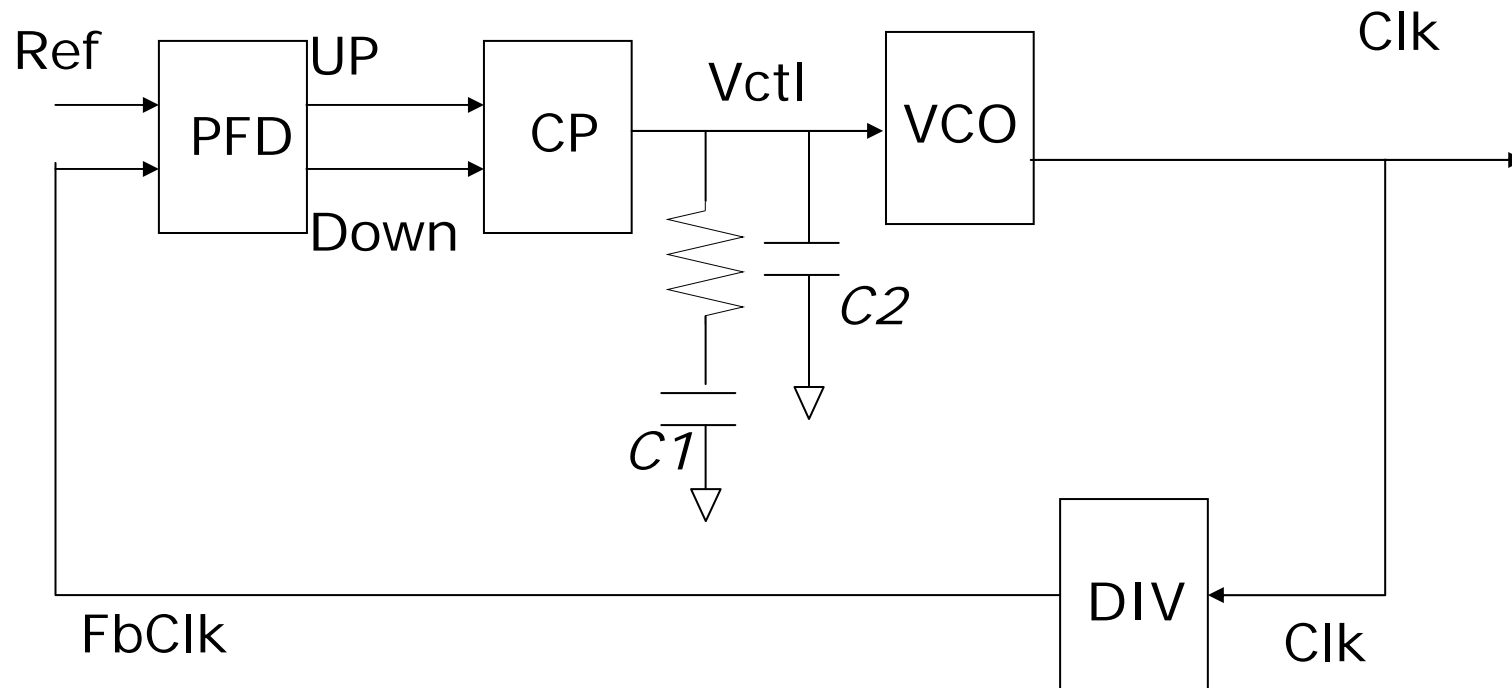

Components in a Nutshell

- PFD: outputs digital pulse whose width is proportional to phase error
- CP: converts digital error pulse to analog error current
- LPF: integrates (and low-pass filters) error current to generate VCO control voltage
- VCO: low-swing oscillator with frequency proportional to control voltage
- DIV: divides VCO clock to generate FBCLK clock


Is My PLL Stable?

- PLL is 2nd-order system similar to mass-spring-dashpot or RLC circuit.
- PLL may be stable or unstable depending on phase margin (or damping factor).
- Phase margin is determined from linear model of PLL in frequency-domain.
- Find phase margin/damping using MATLAB, loop equations, or simulations.
- Stability affects phase error, settling, jitter.

What Does PLL Bandwidth Mean?

- PLL acts as a low-pass filter with respect to the reference signal.
- Low-frequency reference modulation (e.g. spread-spectrum clocking) is passed to the VCO signal.
- High-frequency reference jitter is rejected.
- “Bandwidth” is the frequency at which the PLL begins to lose lock with the reference (-3dB).
- PLL acts as a high-pass filter wrt VCO noise.
- Bandwidth affects phase error, settling, jitter.

PLL Linear Model

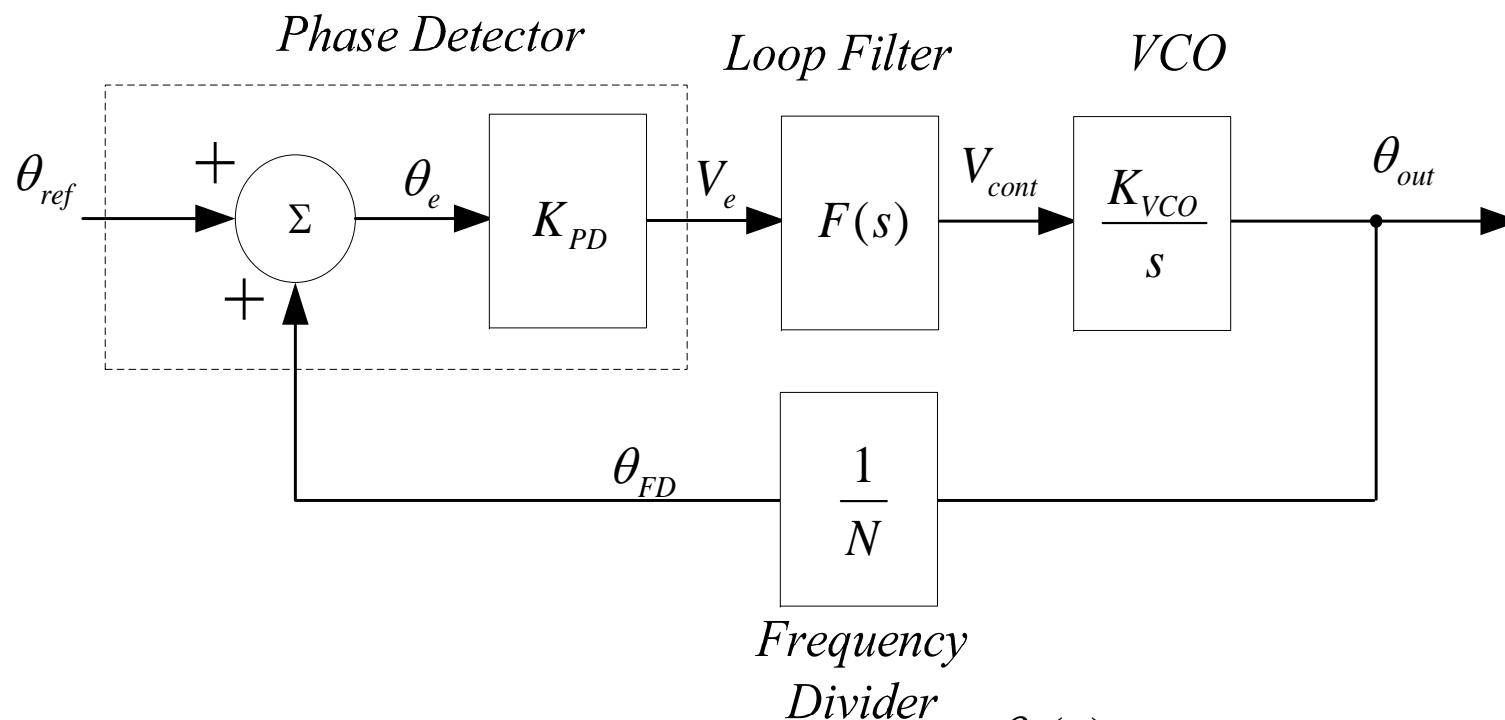

$$H(s) = \frac{\theta_{out}(s)}{\theta_{ref}(s)} = \frac{K_{PD}K_{VCO}F(s)}{s + \frac{K_{PD}K_{VCO}F(s)}{N}}$$

$$\frac{\theta_e(s)}{\theta_{ref}(s)} = \frac{s}{s + \frac{K_{PD}K_{VCO}F(s)}{N}}$$

PLL Linear Model


$$F(s) = \frac{1}{(1 + sRC)}$$

$$H(s) = \frac{\theta_{out}(s)}{\theta_{ref}(s)} = \frac{NK_{PD}K_{VCO}}{s^2 NRC + sN + K_{PD}K_{VCO}}$$

$$H(s) = \frac{N\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

$$\omega_n = \sqrt{\frac{K_{PD}K_{VCO}}{NRC}}$$
 
$$\xi = \frac{1}{2} \sqrt{\frac{N}{K_{PD}K_{VCO}RC}}$$




PLL Linear Model

$$F(s) = \frac{1 + \tau_2 s}{1 + \tau_1 s} \quad \begin{aligned} \tau_1 &= (R_1 + R_2)C \\ \tau_2 &= R_2 C \end{aligned}$$

$$H(s) = \frac{s\omega_n \left(2\xi - \frac{N^2 \omega_n}{K_{PD} K_{VCO}} \right) + N\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

 
$$\omega_n = \sqrt{\frac{K_{PD} K_{VCO}}{N\tau_1}} \quad \xi = \frac{1}{2} \sqrt{\frac{K_{PD} K_{VCO}}{N\tau_1} \left(\tau_2 + \frac{N}{K_{PD} K_{VCO}} \right)}$$



What Determines Stability and Bandwidth?

- Damping Factor (measure of stability)
- Natural Frequency (measure of bandwidth)
- Damping and natural frequency can be set independently by LPF resistor

Noise Model

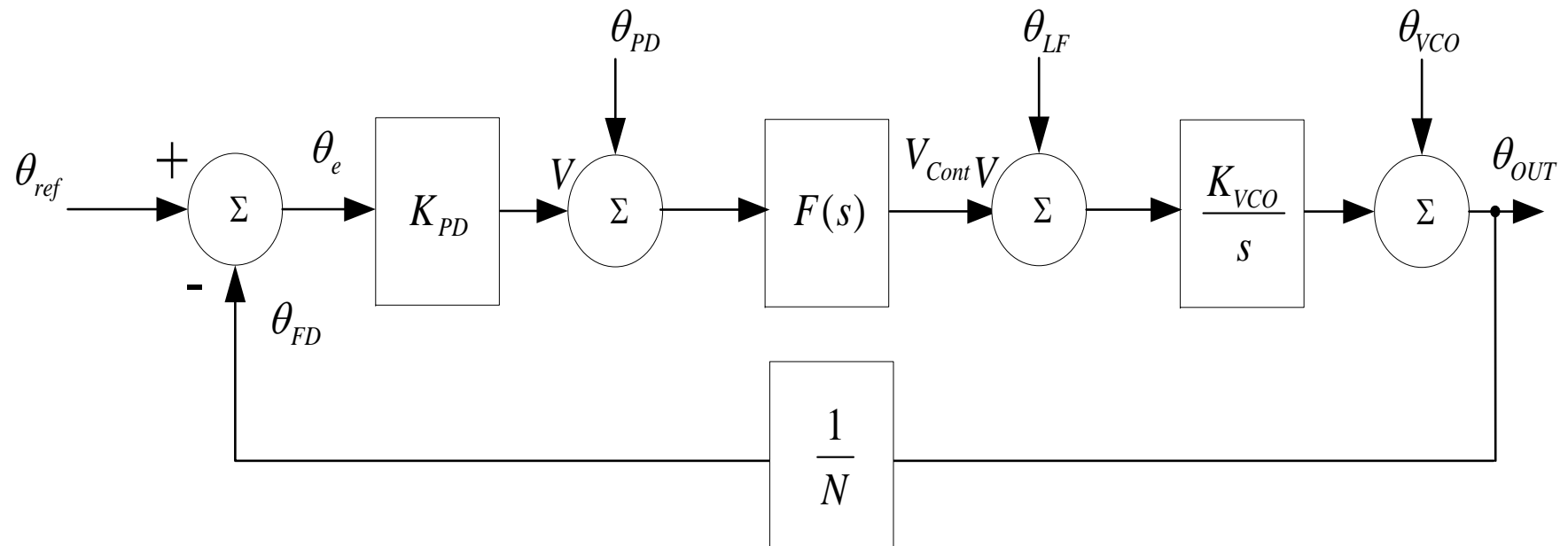

Noise Model---Transfer Functions


$$H(s) = \frac{\theta_{out}(s)}{\theta_{ref}(s)} = \frac{NK_{PD}K_{VCO}F(s)}{Ns + K_{PD}K_{VCO}F(s)}$$

$$\frac{\theta_{out}(s)}{\theta_{vco}(s)} = \frac{Ns}{Ns + K_{PD}K_{vco}F(s)}$$


$$\frac{\theta_{out}(s)}{\theta_{vco}(s)} = \frac{Ns}{Ns + K_{pd}K_{lf}K_{vco}} = \frac{s}{s + \omega_c}$$

For $F(s)=K_{lf}$

Noise Model

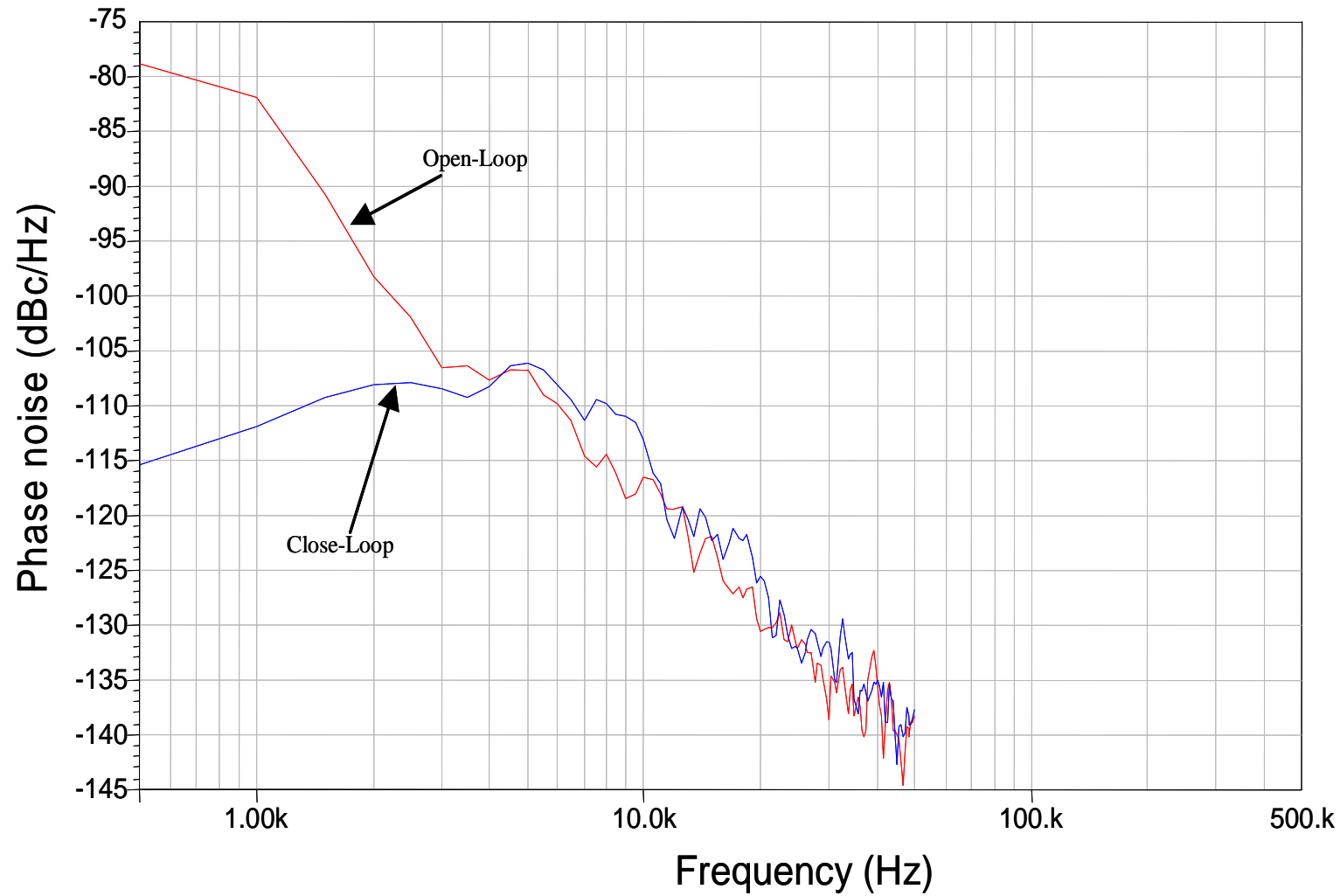

Noise Model

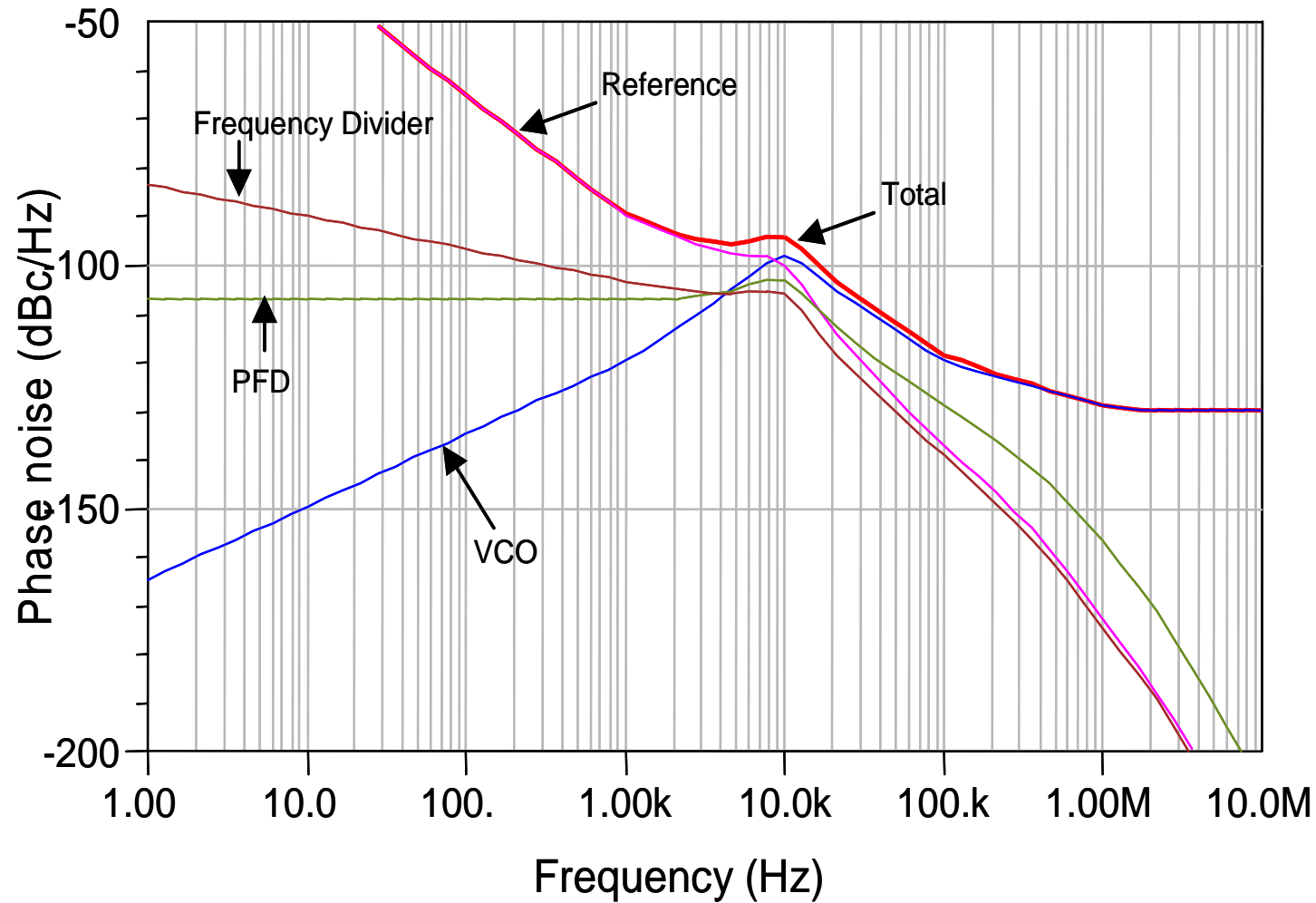


PLL Circuits

- Phase-Frequency Detector
- Charge-Pump
- Low-Pass Filter
- Voltage-Controlled Oscillator
- Voltage Regulator

PFD Block Diagram

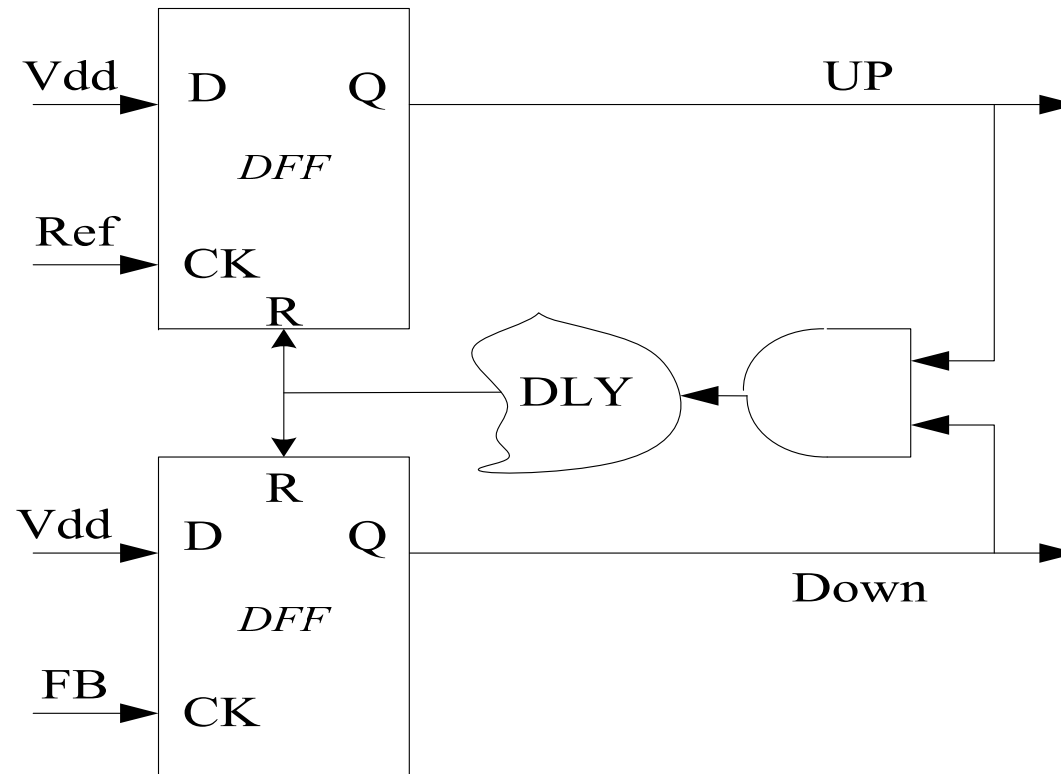Edge-triggered - Input duty-cycle doesn't matter
Pulse-widths proportional to phase error




PFD Logic States

3 and “1/2” Output states
States:

UP	Down	Effect:
0	0	No Change
0	1	Slow Down
1	0	Speed Up
1	1	Avoid Dead-Zone

Example: PFD

 

Avoiding the Dead-Zone

- “Dead-zone” occurs when the loop doesn’t respond to small phase errors - e.g. 10 pS phase error at PFD inputs:
 - PFD cannot generate 10 pS wide *UP* and Down pulses
 - Charge-pump switches cannot turn on and off in 10 pS
 - Solution: delay reset to guarantee min. pulse width (typically > 150 pS)


Charge Pump

- Converts PFD phase error (digital) to charge (analog)
- Charge is proportional to PFD pulse widths

$$Q_{cp} = I_{up} * t_{UP} - I_{dn} * t_{Down}$$

- Q_{cp} is filtered/integrated in low-pass filter

Charge Pump

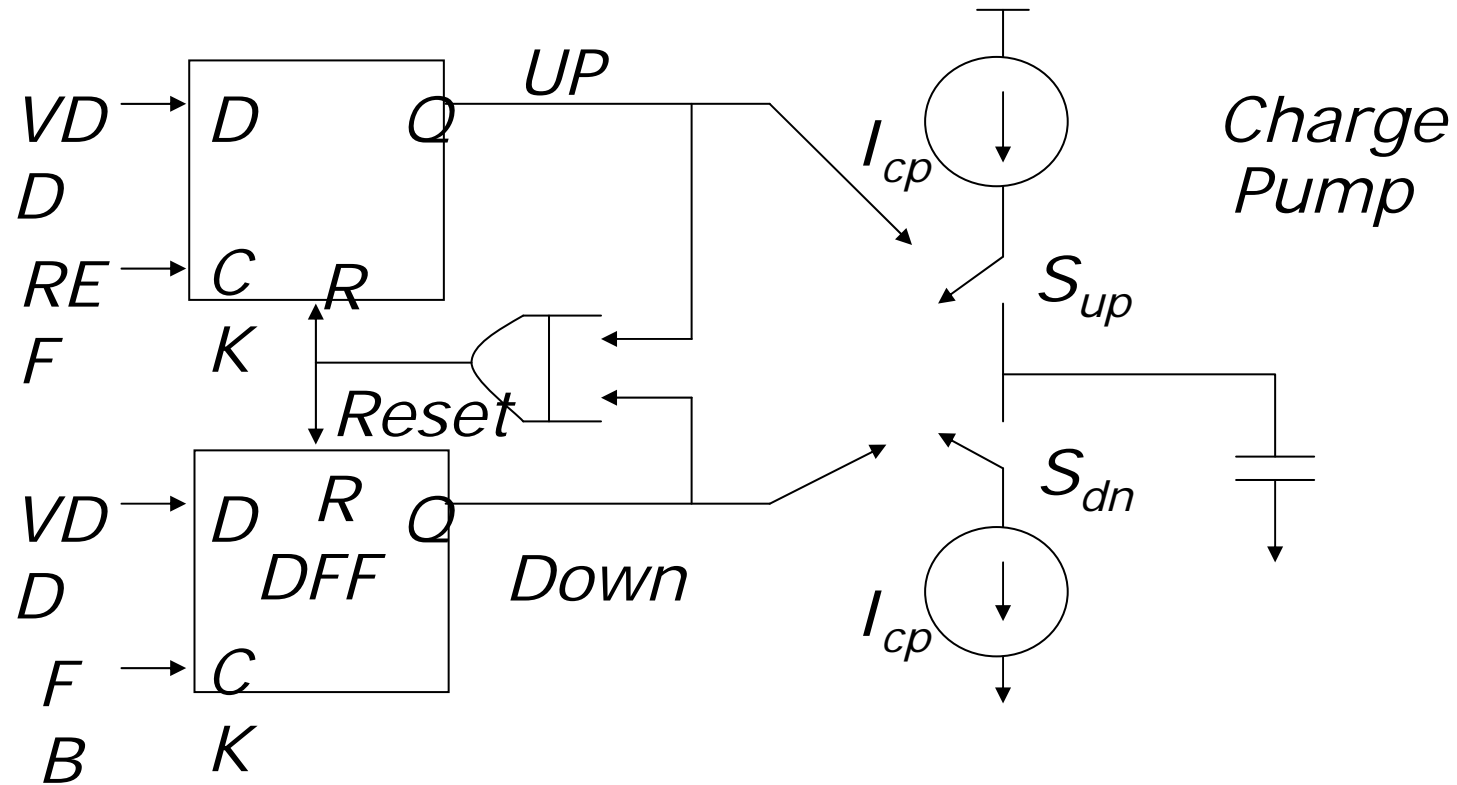

Charge Pump Design Considerations

- Equal *UP/DOWN* currents over entire control voltage range - reduce phase error.
- Minimal coupling to control voltage during switching - reduce jitter.
- Insensitive to power-supply noise and process variations – loop stability.
- Easy-to-design, PVT-insensitive reference current.
- Programmable currents to maintain loop dynamics (vs. M , f_{ref})?
- Typical: $1\mu\text{A}$ (mismatch) $< I_{cp} < 50\mu\text{A}$ (ΔV_{ctl})

Static Phase Error and CP Up/Down Mismatches

- Static Phase Error: in lock, net *UP* and *DOWN* currents must integrate to zero
 - If *UP* current is 2X larger, then *DOWN* current source must be on 2X as long to compensate
 - Feedback clock must lead reference for *DOWN* to be on longer
 - $T_{err} = T_{dn} - T_{up} = T_{reset} * (I_{up}/I_{dn} - 1)$

Static Phase Error and CP Up/Down Mismatches


- Phase error can be extremely large at low VCO frequencies (esp. if self-biased) due to mismatch in current mirrors (low $V_{gs} - V_t$)
- Increase V_{gs} or decrease ΔV_t (large $W*L$)
- Typical static phase error < 100 pS

VCO Jitter and CP Up/Down Mismatches

- PFD-CP correct at rate of reference (e.g. 10nS).
- Most phase error correction occurs near reference rising edge and lasts < 200 pS, causing a control voltage ripple.
- This ripple affects the VCO cycles near the reference more than VCO cycles later in the ref cycle, causing VCO jitter.
- Typ. Jitter $\ll 1\%$ due to *Up/Down* Mismatches
- Avoid ripple by spreading correction over entire ref cycle.
(Maneatis JSSC '03)


Simple Charge Pump

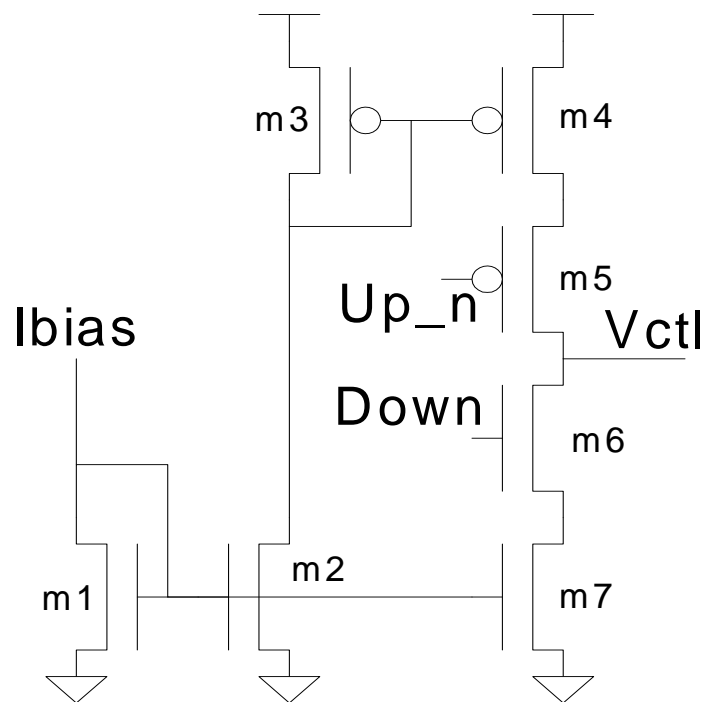- $R(\text{switches})$ varies with V_{ctl} due to body-effect
- Use CMOS pass-gate switches for less V_{ctl} sensitivity
- Long-channel current sources for matching and higher R_{out}




Charge Pump – switches reversed

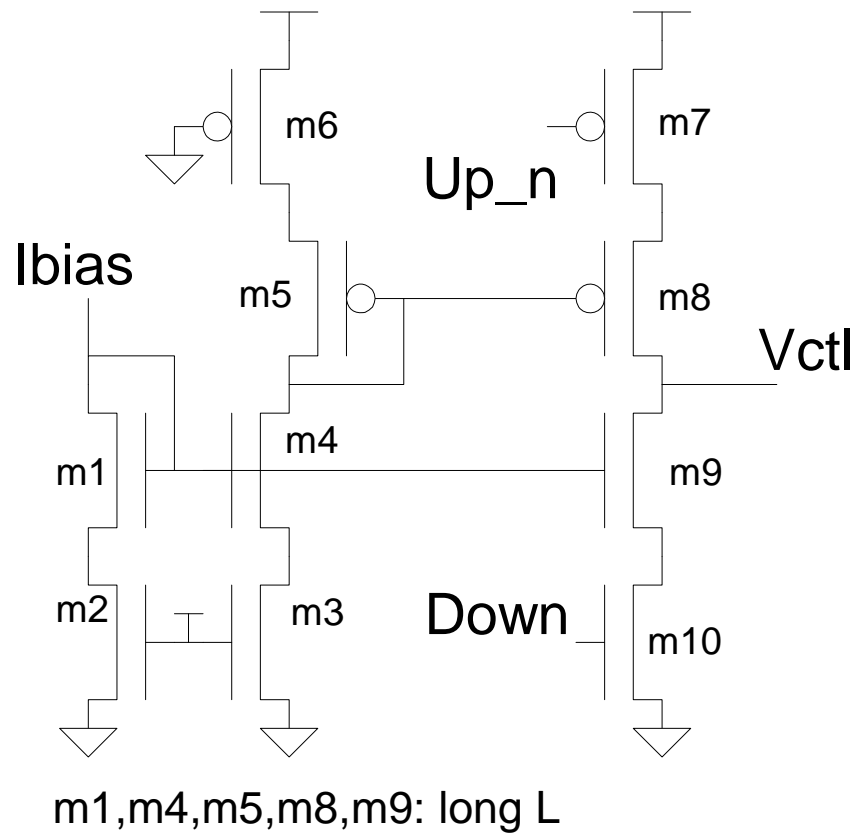- Switches closer to power rails reduce noise and V_{ctl} dependence \rightarrow I_{cp} not constant with up/down



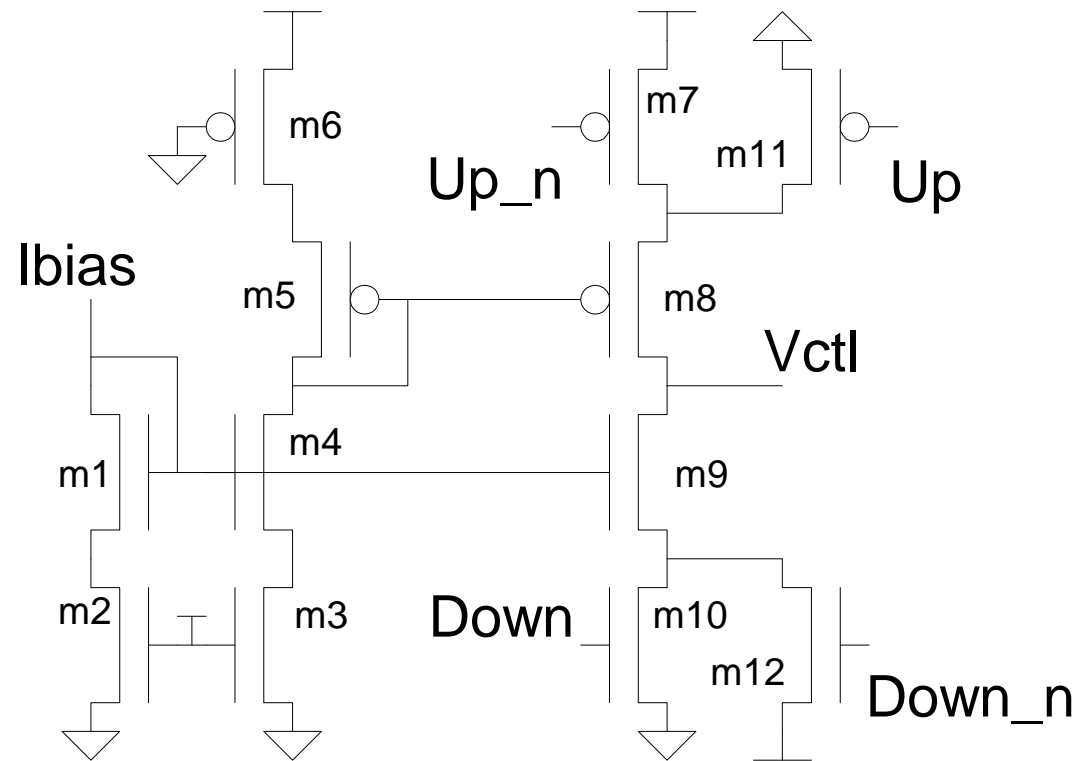Charge Pump: switches reversed with fast turn-off




m1,m4,m5,m8,m9: long L
m11, m12: faster turn-off

(Ingino '01)


Simple Charge-Pump Bias

 - $I_b \sim (V_{dd} - V_t)/R$
- I_b dependent on PVT
- Prefer low- V_t , moderate-to-long L for process insensitivity, large W/L for low gate-overdrive
- Pro: Simple, stable. Con: V_{dd} dependence




VDD-Independent I_{bias}

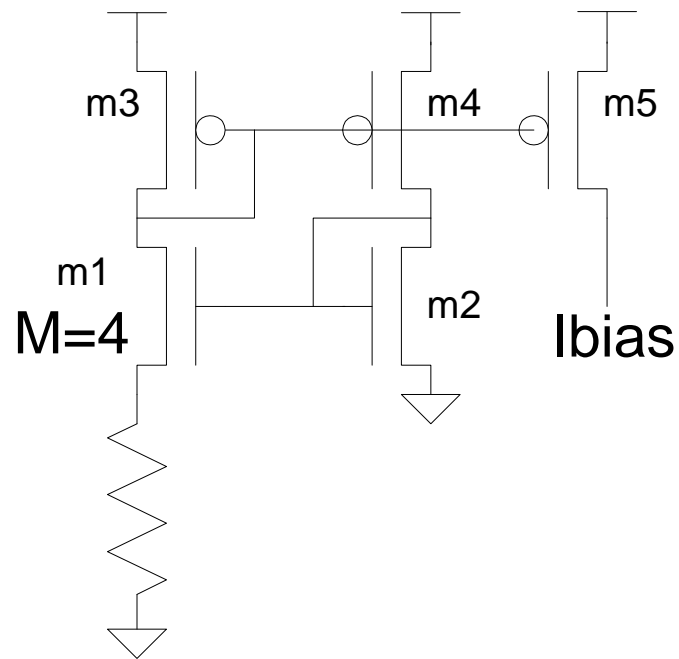- $I_b \sim 1/R_2$
- Con: requires start-up circuit not shown




Bandgap-Based Ibias

 - $I_b \sim V_{ref}/R$
- Con: feedback loop may oscillate
 - cap added to improve stability
- Pro: VDD-independent, mostly Temp independent



Low-Pass Filter

 
- Integrates charge-pump current onto $C1$ cap to set average VCO frequency (“integral” path).
- Resistor provides instantaneous phase correction w/o affecting avg. freq. (“proportional” path).
- $C2$ cap smoothes large IR ripple on V_{ctl}
- Typical value: $0.5k < R_{lpf} < 20k\Omega$



Low-Pass Filter Smoothing Cap(C_2)

- “Smoothing” capacitor on control voltage filters CP ripple, but may make loop unstable
- Creates parasitic pole: $\omega_p = 1/(R C_2)$
- $C_2 < 1/10 * C_1$ for stability
- $C_2 > 1/50 * C_1$ for low jitter
- Smoothing cap reduces “IR”-induced VCO jitter to $< 0.5\%$ from 5-10%
- $\Delta f_{vco} = K_{vco} I_{cp} T_{err} / C_2$
- Larger C_2/C_1 increases phase error slightly

Low-Pass Filter Smoothing Cap(C_2)

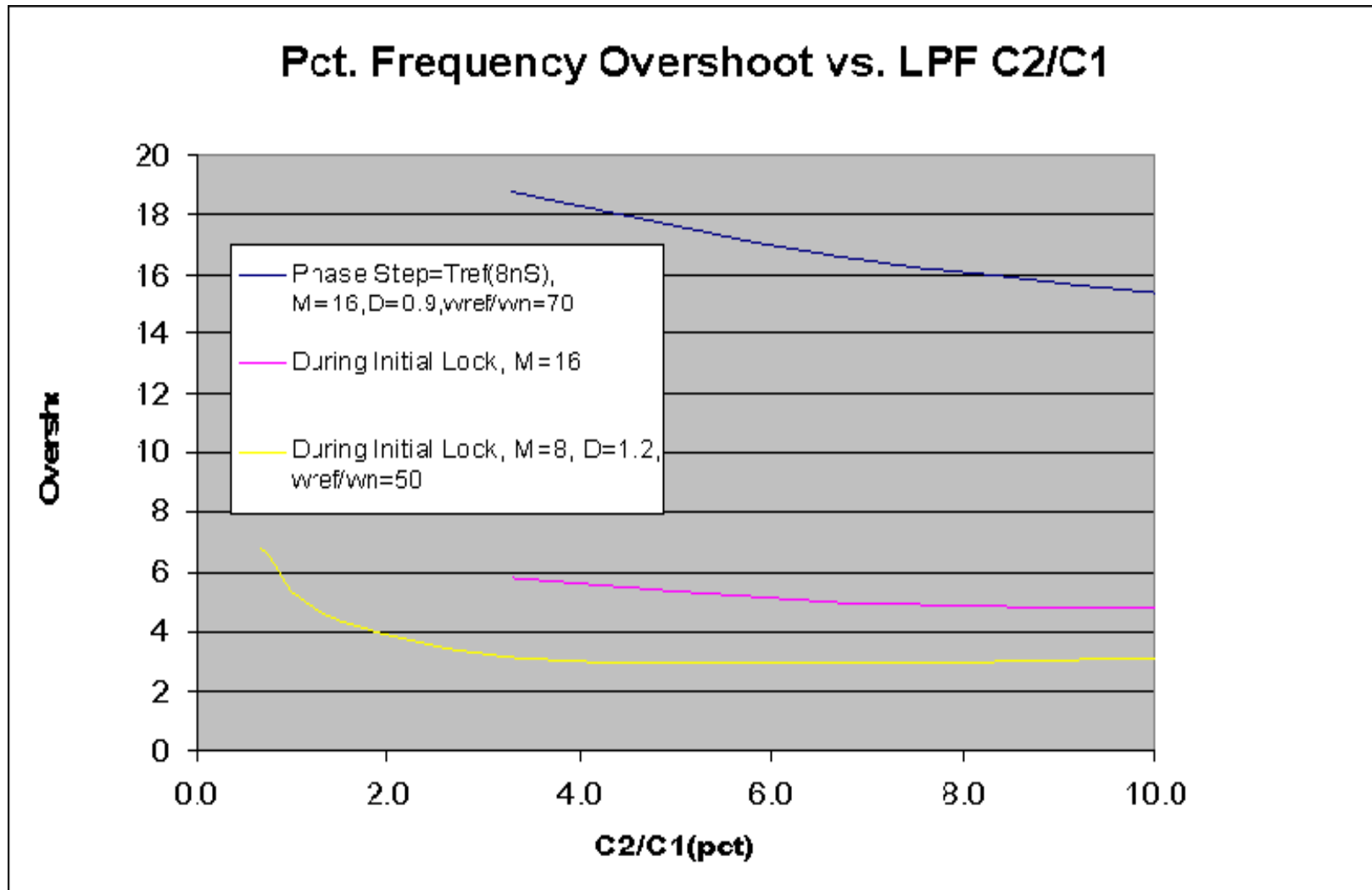

Low-Pass Filter Capacitors

- Even thick gate oxide may still leak too much
- Large filter cap (C_1) typically ranges from 50pF to 400 pF
- C_1 cap BW may be as low as $\sim 10X$ PLL BW for nearly ideal behavior
- Min C_2 BW set by T_{ref}
- Cap BW $\sim 1/RC \sim 1/L^2$
- Gate cap not constant with V_{gs}

PLL Suppression of VCO Noise

- PLL acts like a high-pass filter in allowing VCO noise to reach PLL output
- Need noise-immune VCO to minimize jitter
 - Feedback loop cannot react quickly.
- Power-supply noise is largest source of VCO noise

VCO Design Concerns

- Large frequency range to cover PVT variation:
- Single-ended or differential?
- Vco gain ($f_{vco} = K_{vco} * V_{ctl}$) affects loop stability
- More delay stages \rightarrow easier to initiate oscillation
 - Gain(DC) > 2 for 3 stages
 - Gain(DC) $> \sqrt{2}$ for 4 stages

Voltage Regulator/Filter

- Used to filter power-supply noise
typically > 20 dB (10x) PSRR over entire
frequency range
desire 30+ dB
- Secondary purpose is to set precise voltage level
for PLL power supply
usually set by bandgap reference

Bandgap Reference w/Miller Cap

- Stability and PSRR may be poor w/o Miller cap
- Miller cap splits poles. Can also add R in series w/ C_c for more stability (Razavi '00)

