



Introduction to CMOS RF Integrated Circuits Design


VII. Power Amplifiers



Outline

- Functionality
- Figures of Merit
- PA Design
 - Classical Design (Class A, B, C)
 - High-Efficiency Design (Class E, F)
- Matching Network
- Linearity
- T/R Switches

PAs and TRs Switching in Transceiver

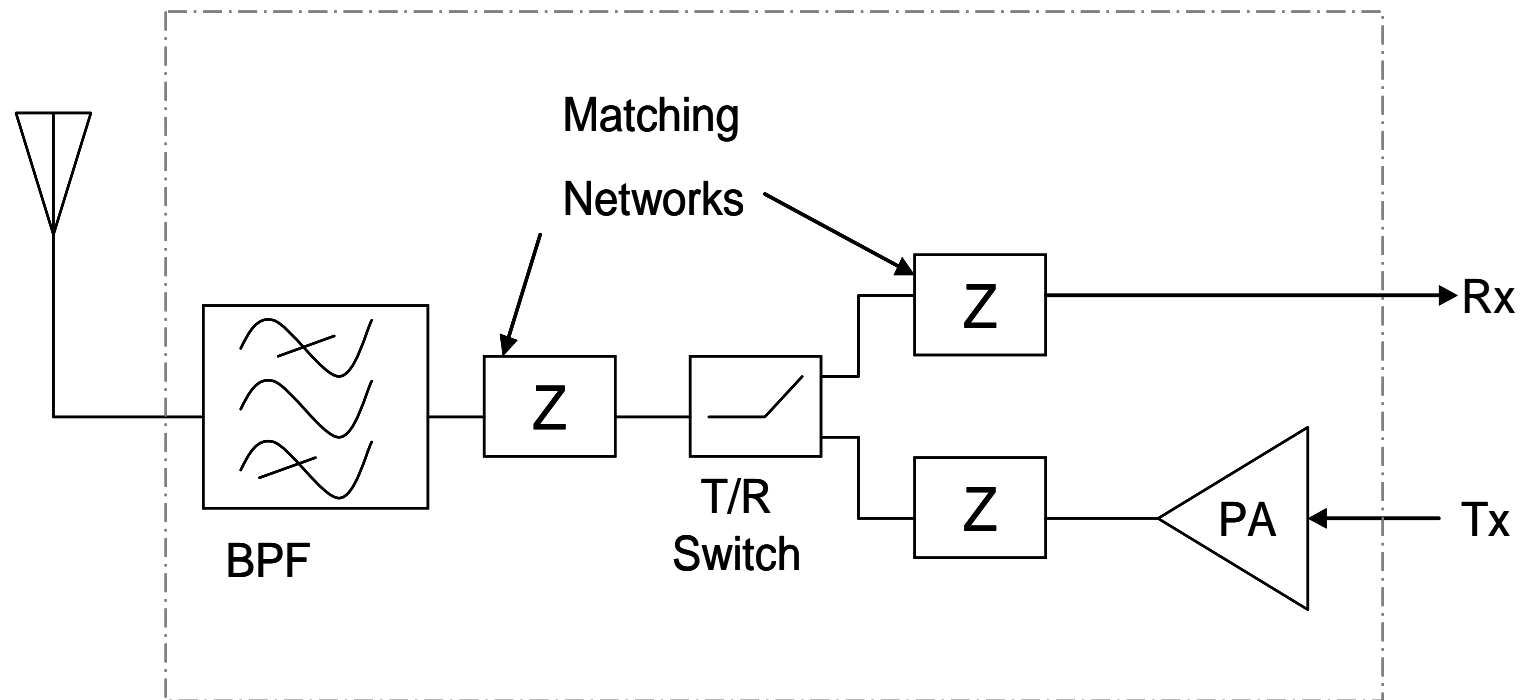

Functionality of PAs

- To Amplify and Deliver Required Signal Power to Antenna at Frequency of Interest
- To Achieve Desired Output Power with Maximum Power Efficiency
- To Provide Output Impedance Matching to Antenna
- To Have Clean Spectrum Not to Affect Receivers

Figures of Merit of PAs

- Frequency
- Output Power
- Power Efficiency
- Linearity (P-1dB, IIP3, ACPR)
- Conversion Gain
- Spur


Output Power

$$P_o = \frac{V_{o,rms}^2}{R_L} = \frac{V_{o,amp}^2}{2R_L} = \frac{V_{o,p-p}^2}{8R_L}$$

- For a Load of 50 Ohm, Need an Output Amplitude of 10 V to Achieve an Output Power of 1W!
- For a Low Supply, Need Small Load for Large Output Power, i.e. A 3.3-V Output Amplitude Can Only Deliver 1W to a Load of 5 Ohm!

Output Power

 - Need an Output Impedance Matching to Convert 50Ω to a Smaller Load!
- As Supply and Load Decrease, PA Would Need to Deliver Much Larger Current
- Loss Due to Parasitic (R, L) Becomes Significant \Rightarrow Low Efficiency!



Power Gain and Efficiency

$$A_p = \frac{P_o}{P_{in}}$$
$$\eta = \frac{P_o}{P_{DC}}$$
$$PAE = \frac{P_o - P_{in}}{P_{DC}}$$


- With a High Power Gain A_p , Drain Efficiency η is Approximately the Same as Power-Added Efficiency PAE

Linearity

- 1-dB Compression Point
- Intermodulation Intercept Point IIP3
- Conventional Definition and Measurement Not Sufficient Because Most PAs Operate Near 1-dB Compression Point for Maximum Efficiency => Higher-Order Distortion Becomes Significant and Needs to Be Included => Adjacent-Channel Power Rejection ACPR

Adjacent-Channel Power Rejection (ACPR)

 - A Modulated Signal is Applied to Include High-Order Distortion
- ACPR is Defined and Measured as the Power of the Adjacent Channel Relative to the Carrier




Typical Figures of Merit

Output Power	$\sim 0 - 35$ dBm
Efficiency	$\sim 30 - 60$ %
Gain	> 20 dB
Linearity, IMD	$- 30$ dBc
Linearity, ACPR	$- 25$ dBc
Spurs	$< - 50$ dBc
Supply Voltage	~ 1.8 V
Current	> 300 mA


Linear Power Amplifiers

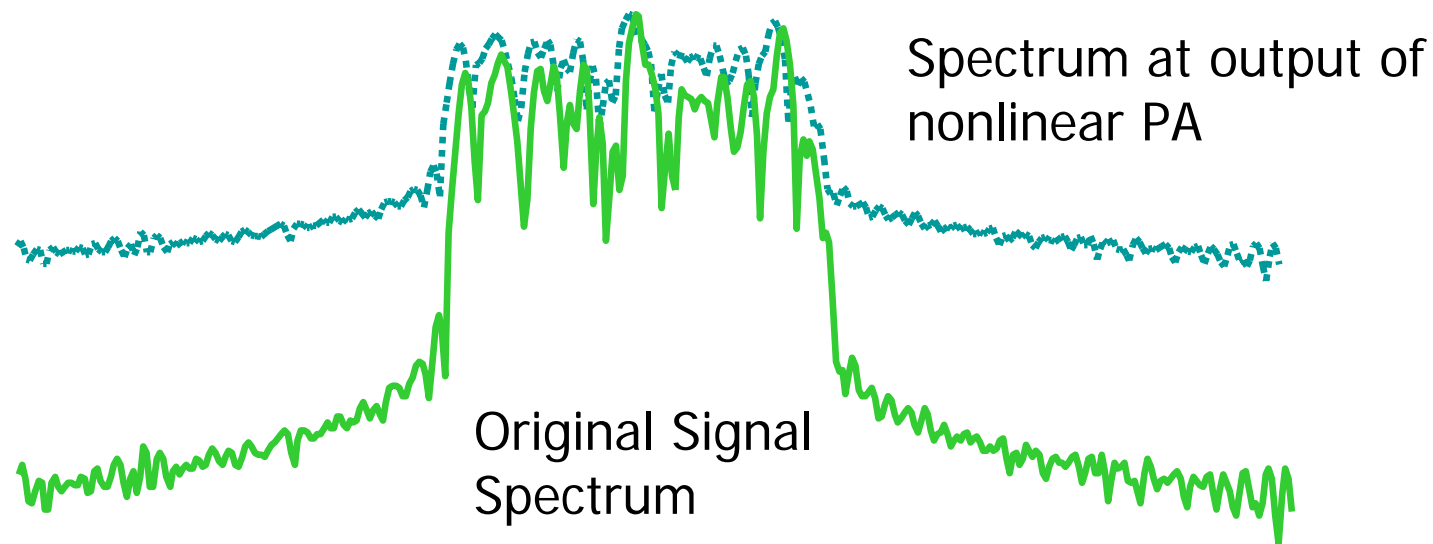- Linear Relationship between Input and Output Signals
- Critical for Applications with Non-Constant Envelope Modulation Scheme
- Classical Linear PAs Include Class-A, Class-B, and Class C
- Classification is Made Based on Conduction Angle, Defined as the Fraction of Period when Active Device is On



Non-Linear Power Amplifiers


Constant envelop
modulation

 

GMSK
FSK

Nonlinear PA
High Efficiency

Nonconstant envelop
modulation

 

BPSK
QPSK
QAM

Linear PA
Low Efficiency

Conduction Angle


$$P_o = \frac{\theta - \sin \theta}{1 - \cos(\theta / 2)}$$

$$\eta = \frac{P_o}{P_{DC}} = \frac{1}{4} \frac{\theta - \sin \theta}{\sin(\theta / 2) - (\theta / 2) \cos(\theta / 2)}$$

Class	A	B	C
θ	360	180	0
η	50%	78%	100%





REF: H. Kraus, et al, *Solid State Radio Engineering*, Wiley, 1980

Conduction Angle

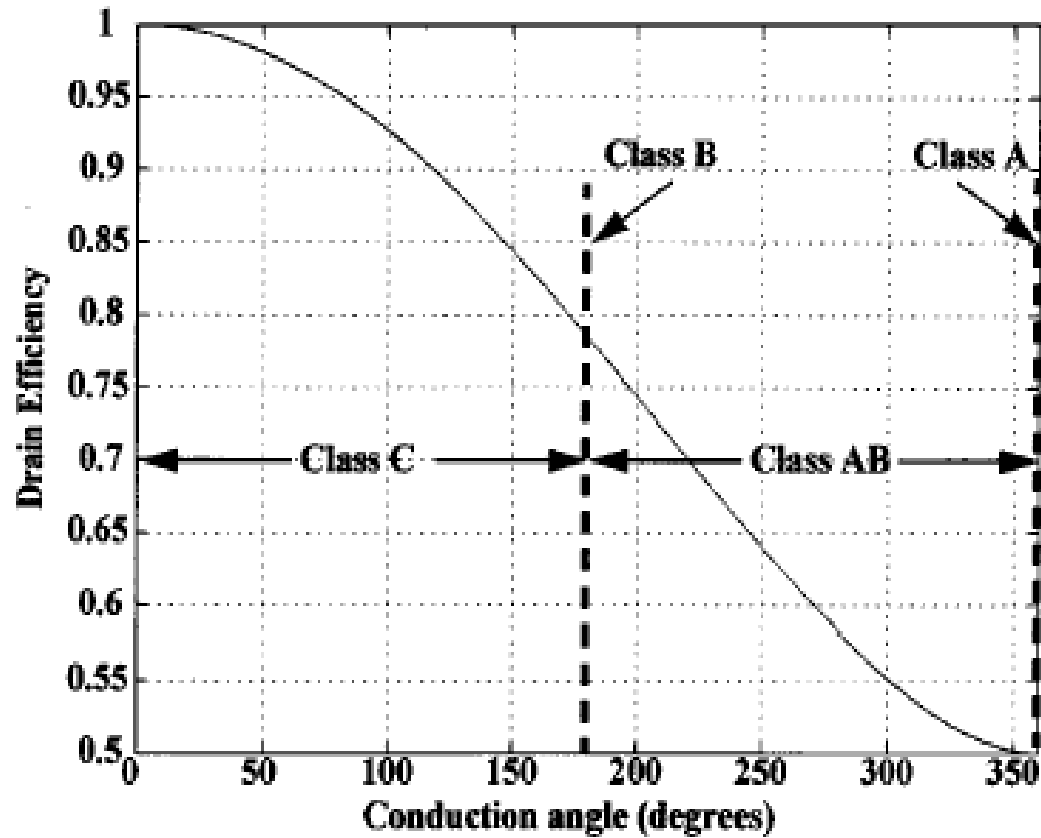

REF: H. Kraus, et al, *Solid State Radio Engineering*, Wiley, 1980

Class-A Power Amplifiers

    

Class-A Power Amplifiers

- Single Transistor as Amplifier to Minimize Loss and Maximize Efficiency
- Transistor Always Conducts \Rightarrow Conduction Angle is 360 Degrees
- Highest Linearity
- Lowest Efficiency


Class-A Power Amplifiers

- RF Choke LC Provides Constant Bias Current Source While Doubling Output Voltage and Efficiency (as Compared to Resistive Load)
- Capacitor C_b Blocks DC Current from Flowing to the Output \Rightarrow No DC Power Consumption for the Load
- Resonant Tank Filters Harmonics Due to Non-Linearity to Obtain Single Tone at Output

Class-A Power Amplifiers

- For Resistive Load, Maximum Output Voltage is Limited to V_{DD}
- For Inductive Load, Maximum Output Voltage is Increased to $2V_{DD}$
 - For Same Loading and Same Supply, Output Power is Increased By 4 Times and Efficiency is Increased By 2 Times
 - For Same Loading and Same Output Power, Supply Can Be Reduced By 2 Times

Class-A PA with Resistive Load

 


$$P_{o,max} = \frac{V_{o,max} I_{o,max}}{2}$$

$$= \frac{V_{DD} I_B}{4}$$

$$P_{DC} = V_{DD} I_{D,ave} = V_{DD} I_B$$

$$\eta_{max} = \frac{P_{o,max}}{P_{DC}} = 25\%$$

Class-A PA with Inductive Load

 





$$P_{o,\max} = \frac{V_{o,\max} I_{o,\max}}{2}$$

$$= \frac{V_{DD} I_B}{2}$$

$$P_{DC} = V_{DD} I_{D,ave} = V_{DD} I_B$$

$$\eta_{\max} = \frac{P_{o,\max}}{P_{DC}} = 50\%$$

Class-B Power Amplifiers

   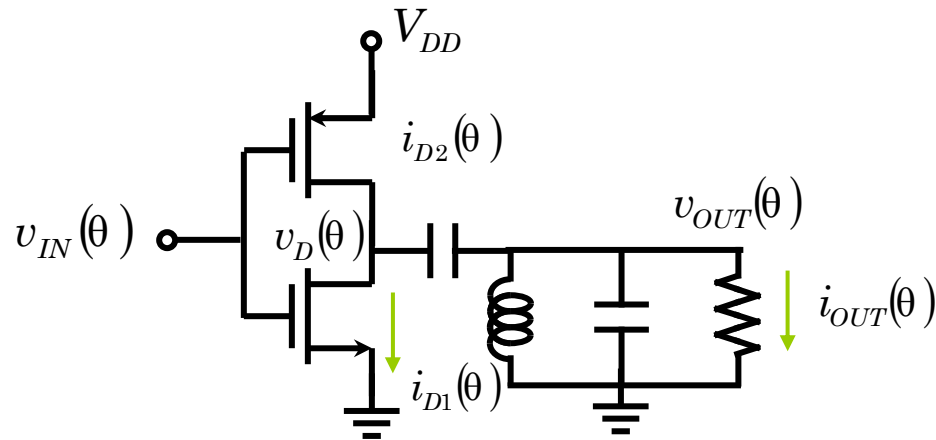

$$P_{RFout} = \frac{V_{om}^2}{2R} \leq \frac{V_{DD}^2}{2R}$$

$$I_{DC} = \frac{1}{2\pi} \int_0^{2\pi} I_D |\sin\theta| d\theta = \frac{2I_D}{\pi} = \frac{2V_{om}}{\pi R}$$

$$\eta_{Drain} = \frac{P_{RFout}}{P_{DC}} = \frac{\frac{V_{om}^2}{2R}}{\frac{2V_{om}}{\pi} \frac{V_{DD}}{R}} = \frac{\pi V_{om}}{4V_{DD}} \leq \frac{\pi}{4} \approx 0.785$$

Class-B Power Amplifiers

- Two Transistors as Push-Pull Amplifier
- Transistors Conduct Only HALF CYCLE => Conduction Angle is 180 Degrees
- Higher Efficiency Compared to Class-A
- Compromised Linearity
- Due to Speed Limitation of PMOS, Two NMOS Can Be Used In Parallel with Their Currents Combined By a Transformer

Class-B Power Amplifier



$$P_{o,\max} = \frac{V_{o,\max} I_{o,\max}}{2} = \frac{V_{DD}^2}{4R_L}$$

$$I_{D,\text{ave}} = \frac{V_{DD}}{\pi R_L}$$

$$P_{DC} = V_{DD} I_{D,\text{ave}} = \frac{V_{DD}^2}{\pi R_L}$$


$$\eta_{\max} = \frac{P_{o,\max}}{P_{DC}} = \frac{\pi}{4} = 78\%$$

Class-C Power Amplifiers

  

$$P_{RFout} \propto \frac{\vartheta - \sin\vartheta}{1 - \cos(\vartheta/2)}$$
 
$$\eta_{Drain} = \frac{P_{RFout}}{P_{DC}} = \frac{1}{4} \frac{\vartheta - \sin\vartheta}{\sin(\vartheta/2) - \frac{\vartheta}{2} \cos(\vartheta/2)}$$



Class-C Power Amplifiers

- Transistor Conducts Much Less Than Half of Cycle => Conduction Angle is Close to Zero Degree
- Higher Efficiency Compared to Class-A and Class-B
- Much Degraded Linearity
- Lower Output Power


Non-Linear Power Amplifiers

- Operate Active Devices as Switches Instead of Amplifying Linear Devices
- Highly Non-Linear
- Highest Efficiency ($\sim 100\%$)
- Most Suitable for Applications with Constant-Envelope Modulation
- For Linear Applications, Need Linearization Techniques
- Includes Class-E, Class-F



Non-Linear Power Amplifiers

- In Practice, Efficiency is Limited to $\sim 60\%$ Due to:
 - High Speed \Rightarrow Not Too Large Device Size \Rightarrow Finite Turn-On Resistance of the Switch
 - Finite Turn-On Transition Times
 - Low-Q Inductors \Rightarrow Off-Chip Inductors or Bond Wires
- For High Output Power, Device Stress is Critical

Class-E Power Amplifiers

 

 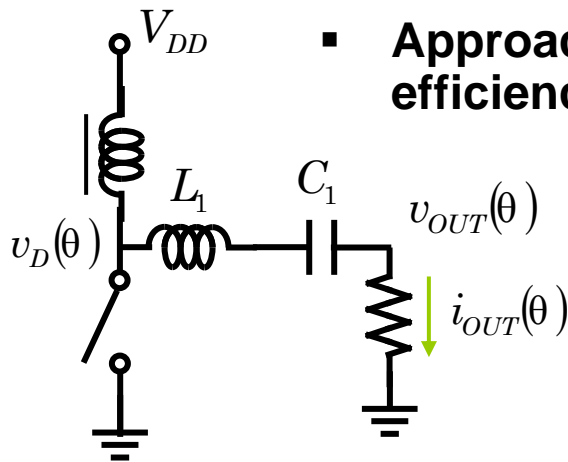
- **Switch mode**
- **Approaching 100% efficiency**



Class-E Power Amplifiers

- Operate Active Device as Switch To Minimize Power Loss and Maximize Efficiency ($\sim 100\%$):
 - Small Transition Times Between ON and OFF
 - Small Voltage when Conducting Current
 - Small Current when Sustaining Large Voltage
 - Change of Voltage with Time is Close to Zero when Starting Conducting
- Parasitic Capacitance of Device Can Be Conveniently Absorbed in C_d

Class-E Power Amplifiers


 


$$L_r = \frac{\pi V_{DD}^2 (\pi^2 - 4)}{2\omega (\pi^2 + 4)}$$



$$C_d = \frac{P_o}{\pi\omega V_{DD}^2}$$

$$R_{opt} = 0.58 \frac{V_{DD}^2}{P_o}$$

Class-F Power Amplifiers

 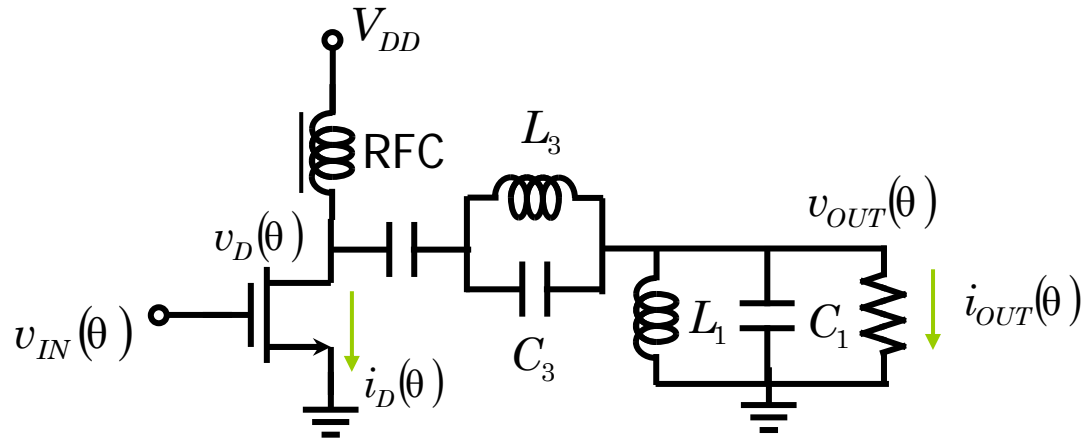

  - L_3C_3 tuned to the 2nd or 3rd harmonics
- Peak efficiency
 - 88% for 3rd harmonics peaking
 - 85% for 2nd harmonics peaking.



Class-F Power Amplifiers

- Employ Harmonics to Simulate a Square Waveform to Minimize Transition Times and thus to Reduce Loss
- A Parallel Tank $Lr3Cr3$ is Included to Obtain a Third-Order Harmonic and to Add to the Fundamental to Approximate a Square Wave


Challenges for CMOS PAs

- Trade-Off Among All Parameters
 - Speed
 - Device Size
 - Current and Output Power
 - Supply Voltage
 - Loss and Efficiency
 - Device Stress
- Low-Q On-Chip Inductors \Rightarrow Off-Chip Inductors or Bond Wires for Inductors in Resonant Tanks and Matching Network

Linearization Techniques

- Critical for Both High Efficiency and High Linearity
- Use Non-Linear Power Amplifiers (Class E and/or F) for High Efficiency
- Use Linearization Techniques to Improve Linearity:
 - Feed-Forward
 - Envelope Elimination and Restoration

Feed-Forward Techniques

 

Feed-Forward Techniques

$$v_o = v_x - A_v v_y$$

$$v_x = A_v v_{in} + \Delta v$$


$$v_y = \frac{A_v v_{in} + \Delta v}{A_v} - v_{in} = \frac{\Delta v}{A_v}$$

$$\therefore v_o = v_x - A_v v_y = A_v v_{in}$$

Feed-Forward Techniques

- Open Loop Without Feedback \Rightarrow Unconditional Stability
- Limited Linearity Improvement Due to:
 - Gain Mismatches
 - Phase Mismatches
 - Errors of Subtractors
- Can Be Extended to Nested Feed-Forward Loops to Improve Linearity at A Cost of More Complexity

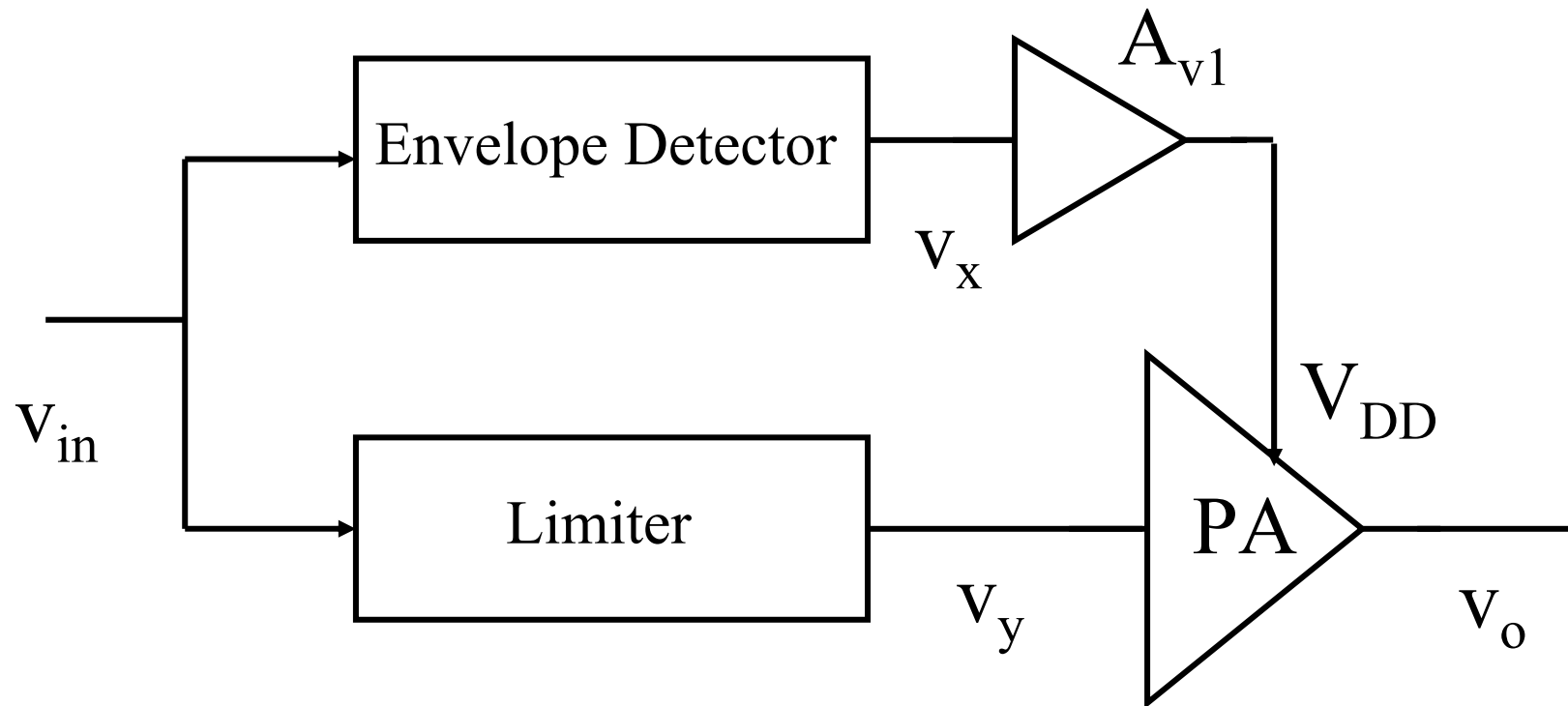Envelope Elimination and Restoration (EER) Techniques



Envelope Elimination and Restoration (EER) Techniques

- Decompose Input Signal into An Envelope and a Phase-Modulated Signal, both of which are Amplified Separately and Recombined
- Constant-Envelope High-Frequency Phase-Modulated Component is Generated by “Eliminating” from Input’s Envelope Using a Limiter and then Applied as Input to a High-Efficiency Switching PA

Envelope Elimination and Restoration (EER) Techniques

- Non-Constant Low-Frequency Envelope Can Be Extracted by an Envelope Detector, Amplified by a Switching Supply Voltage, and then “Recombined” with RF Phase-Modulated Component By Modulating the PA’s Supply Voltage
- Achieve Linearization without Sacrificing Efficiency

Envelope Elimination and Restoration (EER) Techniques

- Operating Frequencies of the Two Paths are Quite Different
- Suffer from Phase and Gain Mismatches \Rightarrow Limited Linearity Improvement
- Power Consumption Can Be High \Rightarrow Power Efficiency Can Be Degraded