



Homework #4


Date: October 22, 2012

Due: October 29, 2012; No late work accepted;

TA: 李哲 Email: justinian@sjtu.edu.cn or lizhe@ic.sjtu.edu.cn

- Use A4 paper to write/print your answer.
- Your name and student ID on the cover page.
- Staple the pages!!!

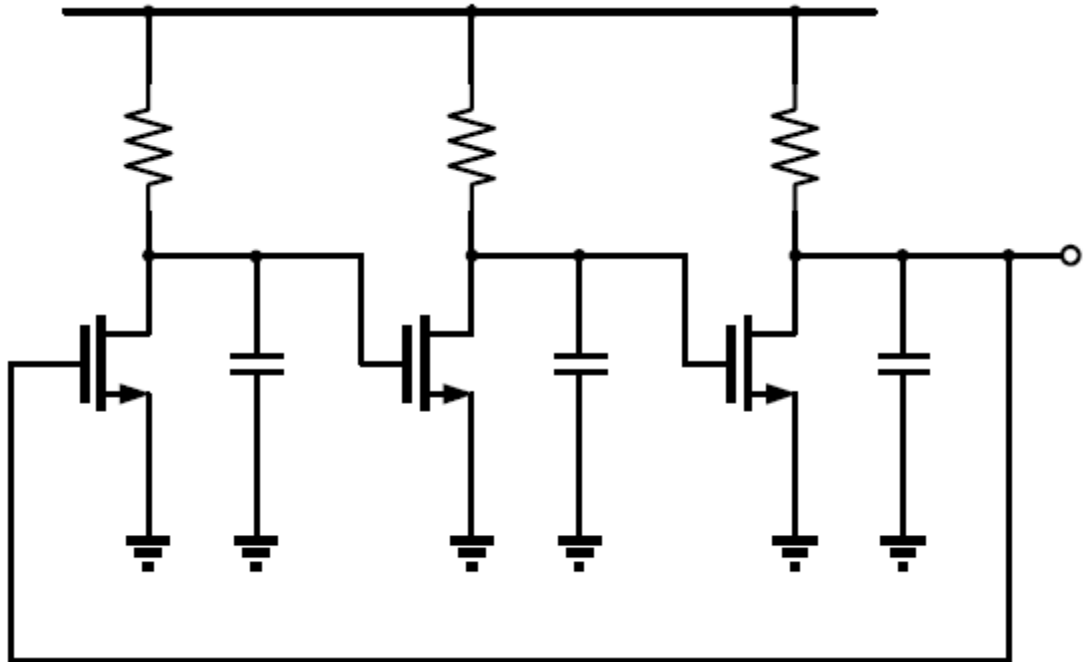1. In the circuit shown below, assume $g_{m1} = g_{m2} = g_{m3} = (200\Omega)^{-1}$
- a) What is the minimum value of R_D that ensures oscillation?
 - b) Determine the value of C_L for an oscillation frequency of 1GHz and a total low-frequency loop gain of 16.





2. With the oscillator shown below.

- a) Assume the voltage swing is large enough to turn MOSFETs on or off suddenly, then drain current of MOSFETs works in a square manner. Explain why output waveforms are closer to sinusoids.
- b) If $L_p=5\text{nH}$ and the total (fixed) parasitic capacitance seen at X (and Y) to ground is 500fF , determine the maximum capacitance than D1 and D2 can add to the circuit.

