

Lab #3: *Design a 8-bit Arithmetic Logic Unit*



8-bit Full Adder Design

TA : JIAO Jiajia

Jun.4, 2013




Outline

- ✦ Background
- ✦ Adder Design
- ✦ Lab3 Introduction
- ✦ Upload the Lab report



Background

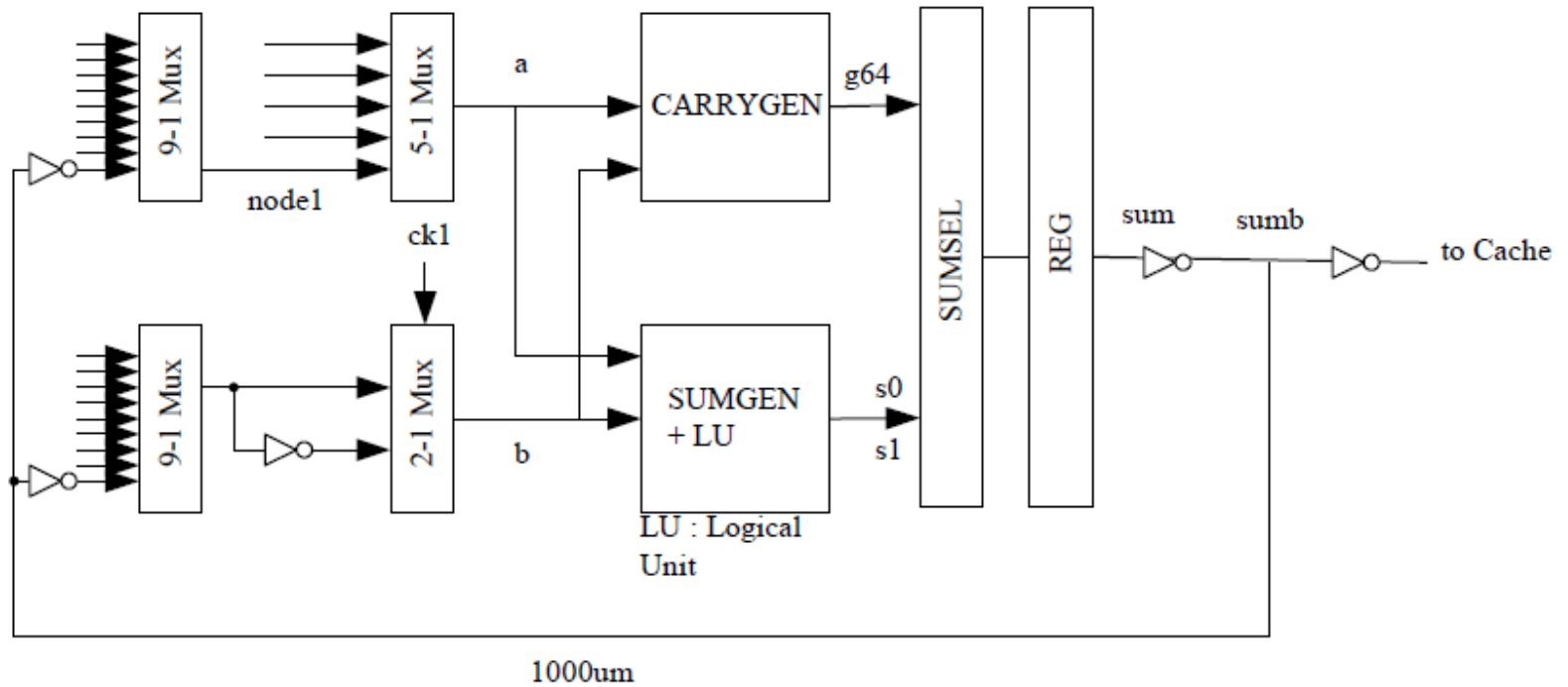

Arithmetic-logic units are the heart of any microprocessor



Background

- ✦ An ALU has four major parts
 - ◆ Arithmetic block
 - ◆ Logic block
 - ◆ Multiplexers
 - ◆ Registers
- ✦ The core of the arithmetic block is an adder




Adder

Half Adder

$$S = A \oplus B$$

$$C_{out} = A \cdot B$$

 

A	B	C_{out}	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

$$S = \overline{A}B\overline{C} + \overline{A}B\overline{C} + \overline{A}B\overline{C} + ABC$$

$$= A \oplus B \oplus C = P \oplus C$$


$$C_{out} = AB + (A + B)C$$

$$= \overline{AB} + \overline{(A + B)C} = MAJ(A, B, C)$$

Full Adder

$$S = A \oplus B \oplus C$$

$$C_{out} = MAJ(A, B, C)$$

 

A	B	C	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

delete

propagate

generate



PGK

- For a full adder, define what happens to carries

- Generate: $C_{out} = 1$ independent of C

- $G = A \cdot B$

$$C_o(G, P) = G + PC_i$$

- Propagate: $C_{out} = C$

- $P = A \oplus B$

$$S(G, P) = P \oplus C_i$$

- Kill: $C_{out} = 0$ independent of C

- $K = \sim A \cdot \sim B$


- Note that we will be sometimes using an alternate definition for

$$\text{Propagate } (P) = A + B$$



Full Adder Design-typical

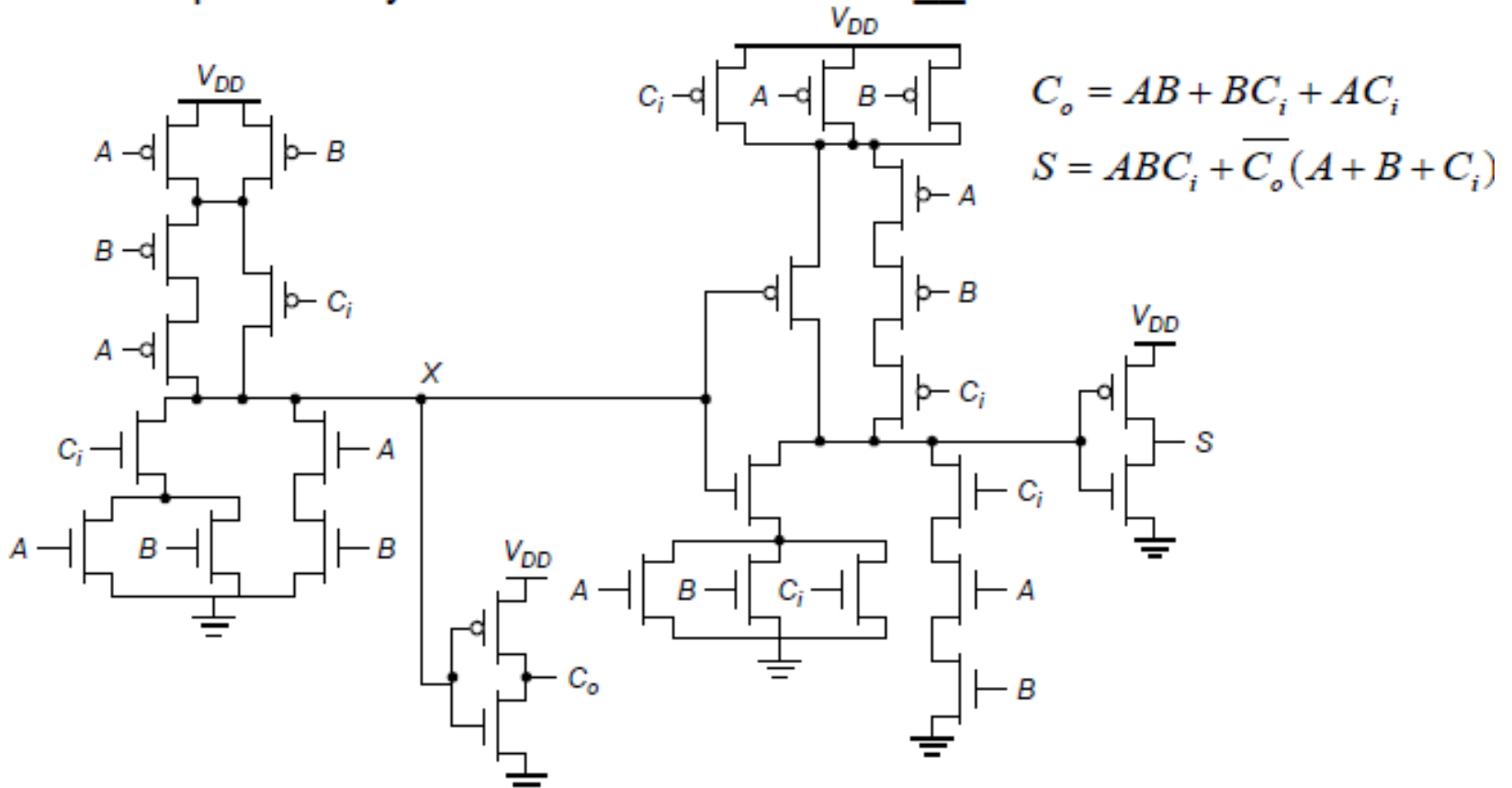Complimentary Static CMOS Full Adder __ 28 Transistors





Multi-bit Full Adder Design

- ✦ Carry-Ripple Adder
- ✦ Carry-Skip Adder
- ✦ Carry-Lookahead Adder
- ✦ Carry-Select Adder
- ✦ Tree Adder



Carry-Ripple Adder

- ✦ A N-bit full adder can be composed of N 1-bit full adder
- ✦ Critical path delay

$$t_{adder} \approx (N - 1)t_{carry} + t_{sum}$$

- ✦ CRA is not suitable for long-word addition due to its propagation delay



Lab3 Introduction



Introduction

✦ Object:

- ◆ Design a 8-bit Full Adder for a 8-bit ALU

✦ You can select any full adder structure and implement it with any circuit family:

- ◆ Complementary Static CMOS
- ◆ Pass-Transistor
- ◆ Dynamic



Design Flow

- ✦ 1. Determine the FA structure
 - ◆ Carry-Ripple Adder(basic)
- ✦ 2. Determine circuit family
 - ◆ Complementary Static CMOS
 - ◆ Pass-Transistor
 - ◆ Dynamic
- ✦ 3. Design the full adder
 - ◆ Single-bit adder(Schematic/MOS size)
 - ◆ Multi-bit adder(Symbol)



Design Flow(cont')

- ✦ 4. Simulation
 - ◆ Functionality
 - ◆ Performance(Delay, power, EDP)
- ✦ 5. Optimize the performance
 - ◆ Size optimization
 - ◆ Structure optimization



LAB Requirements

✦ Basic Part

- ✦ Design a 8-bit carry-ripple adder with any circuit family
- ✦ Verify it and report the performance of your design, including delay, EDP, area(# of transistors)



LAB Requirements

☀ Optional part: Tasks

- ◆ Design your full adder with other circuit families and compare the performance metric EDP by the possible methods:

- Insert the buffers to optimize the stages and transistors size for a smaller transmission latency
- Reduce the V_{dd} to decrease the power consumption
- Combine the structure with other circuit families...

☀ You can choose one or more ways to finish if you have enough time



Tips

✦ log018.scs

◆ Vdd 1.8V

◆ MOS L 180nm

✦ unit

◆ Time eg: input 3n, not 3ns

◆ Cap eg: input 25f, not 25fF

✦ Model Name:

◆ NMOS -- nch PMOS -- pch



Report Requirements

- ✦ Your lab report should include:
 - ✦ Circuit schematic of your design, including your transistor size (you may need to create symbols for your sub-circuits)
 - ✦ Your patterns to verify the full adder and corresponding performance index (Delay, power, EDP)



Report Submit

- ✦ Submit a pdf or word document with name lab3_adder_id_name, eg:
lab3_adder_511...._zhanghua.pdf
- ✦ Upload it to MOODLE system no later than 23:55AM, June 16, 2013(two weeks)



Reference

✦ **Jan M. etc, *Digital Integrated Circuits: A Design Perspective, Second Edition***



Let's Start!

